
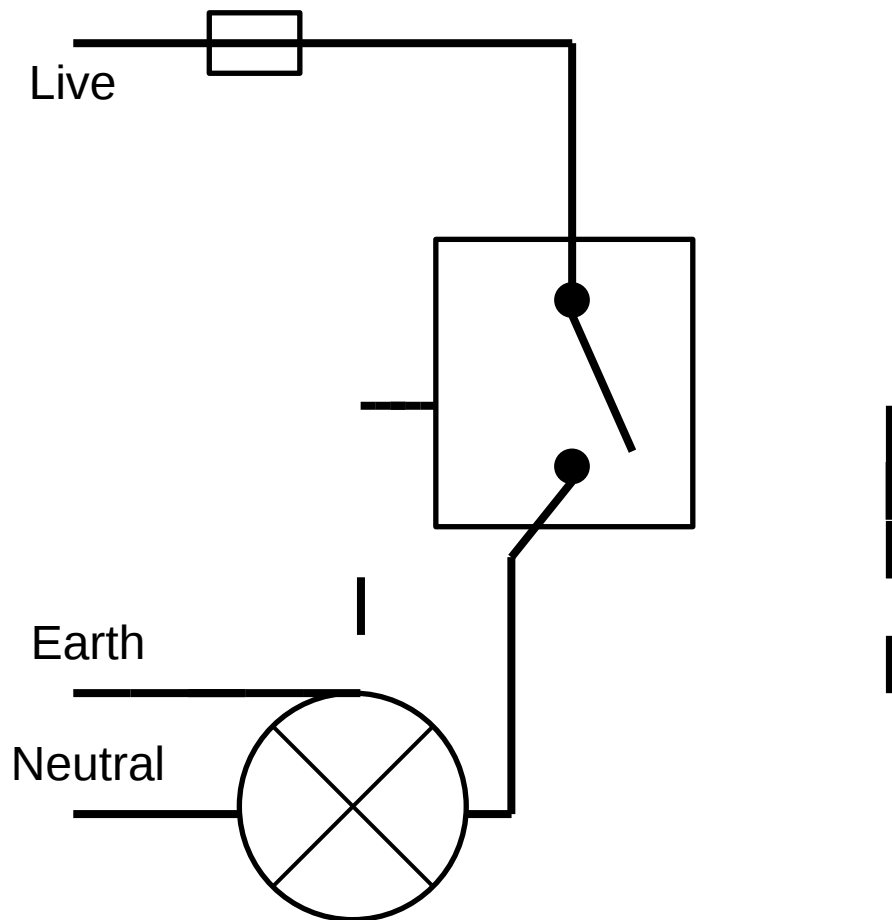



One Way Switching (Circuit Diagram)

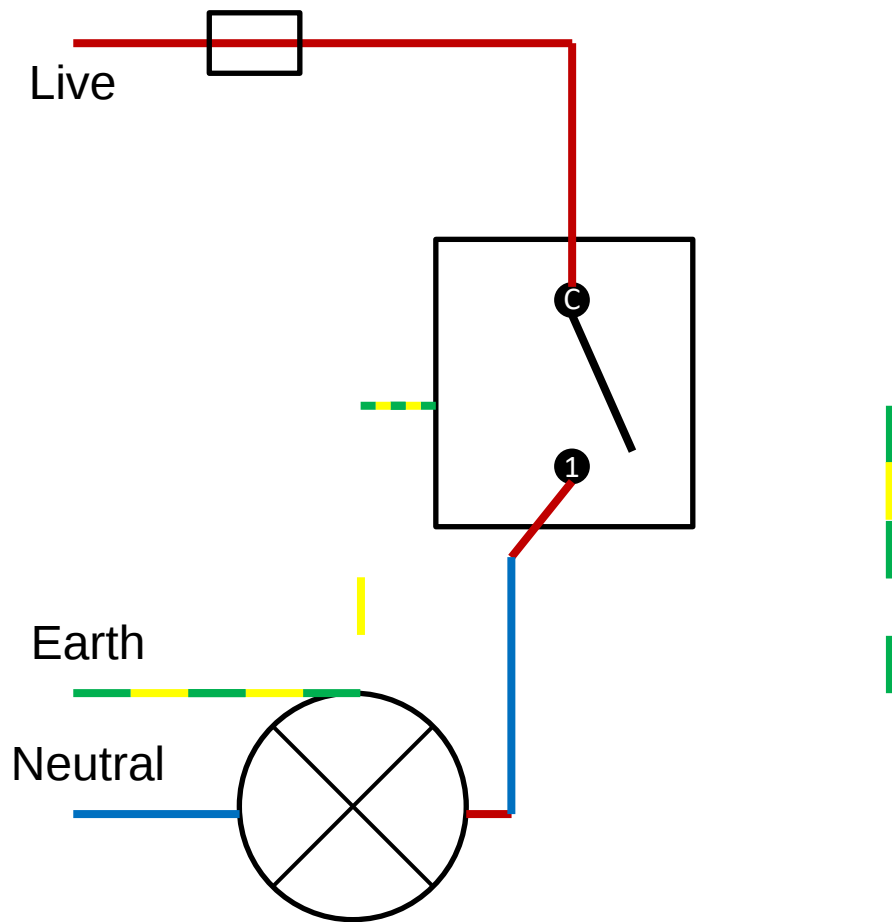


One Way Switching (Wiring Diagram)




One Way Switching

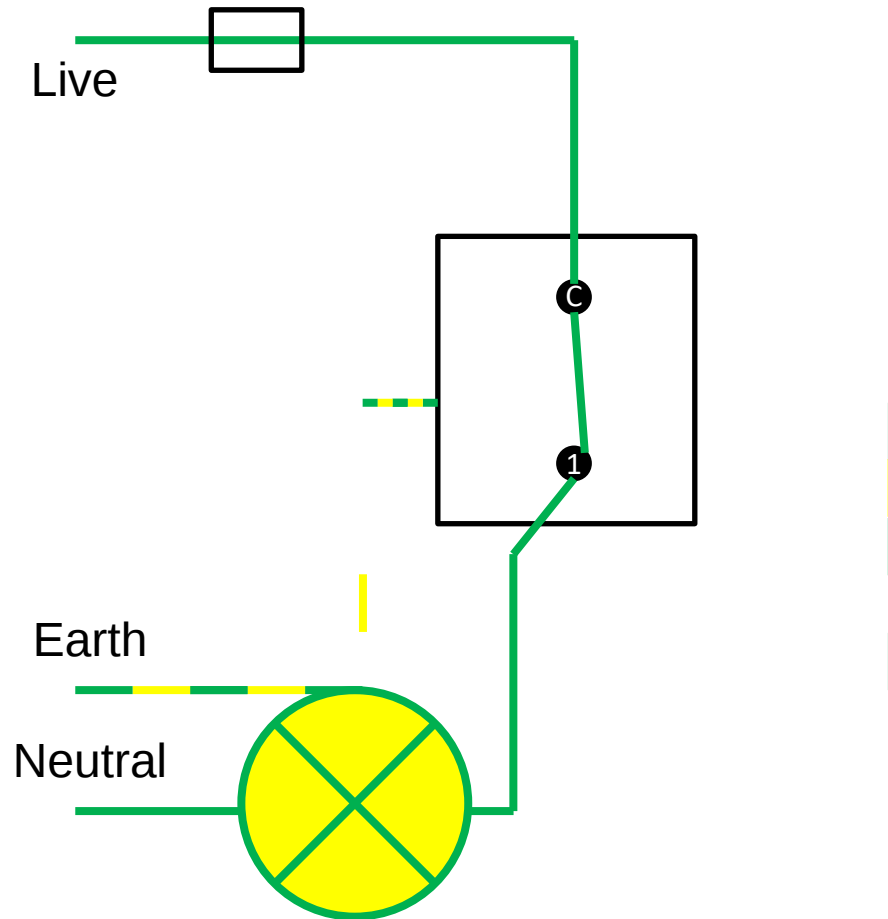


One Way Switching

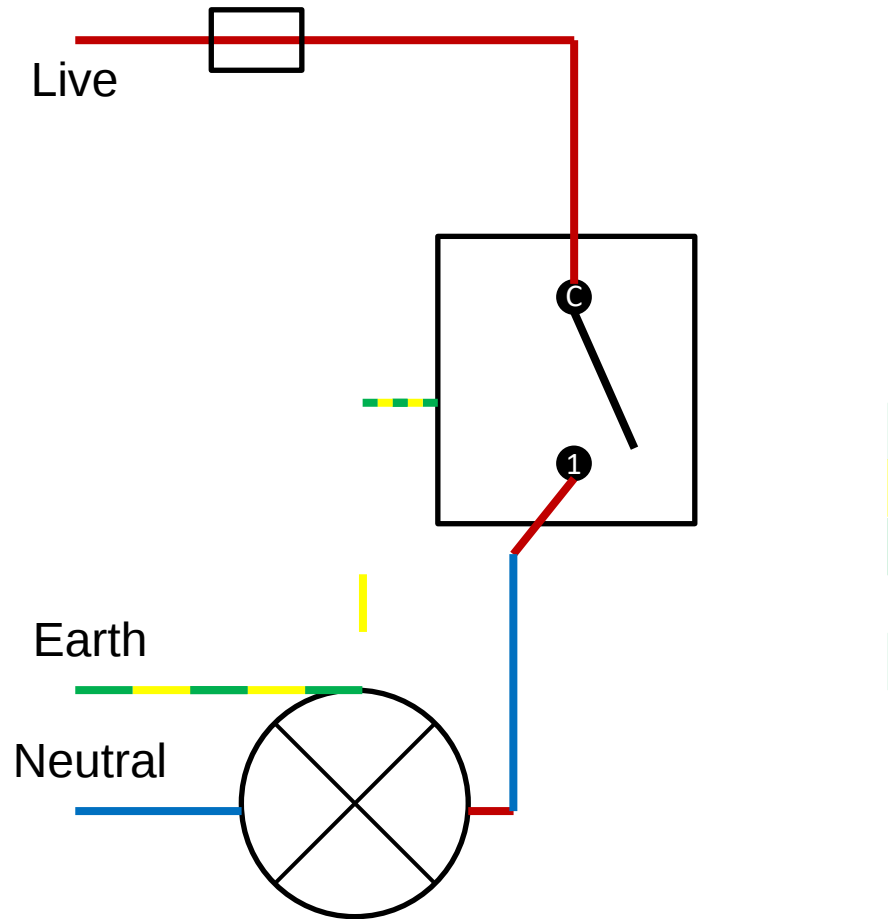


Two Way Switching (Circuit Diagram)

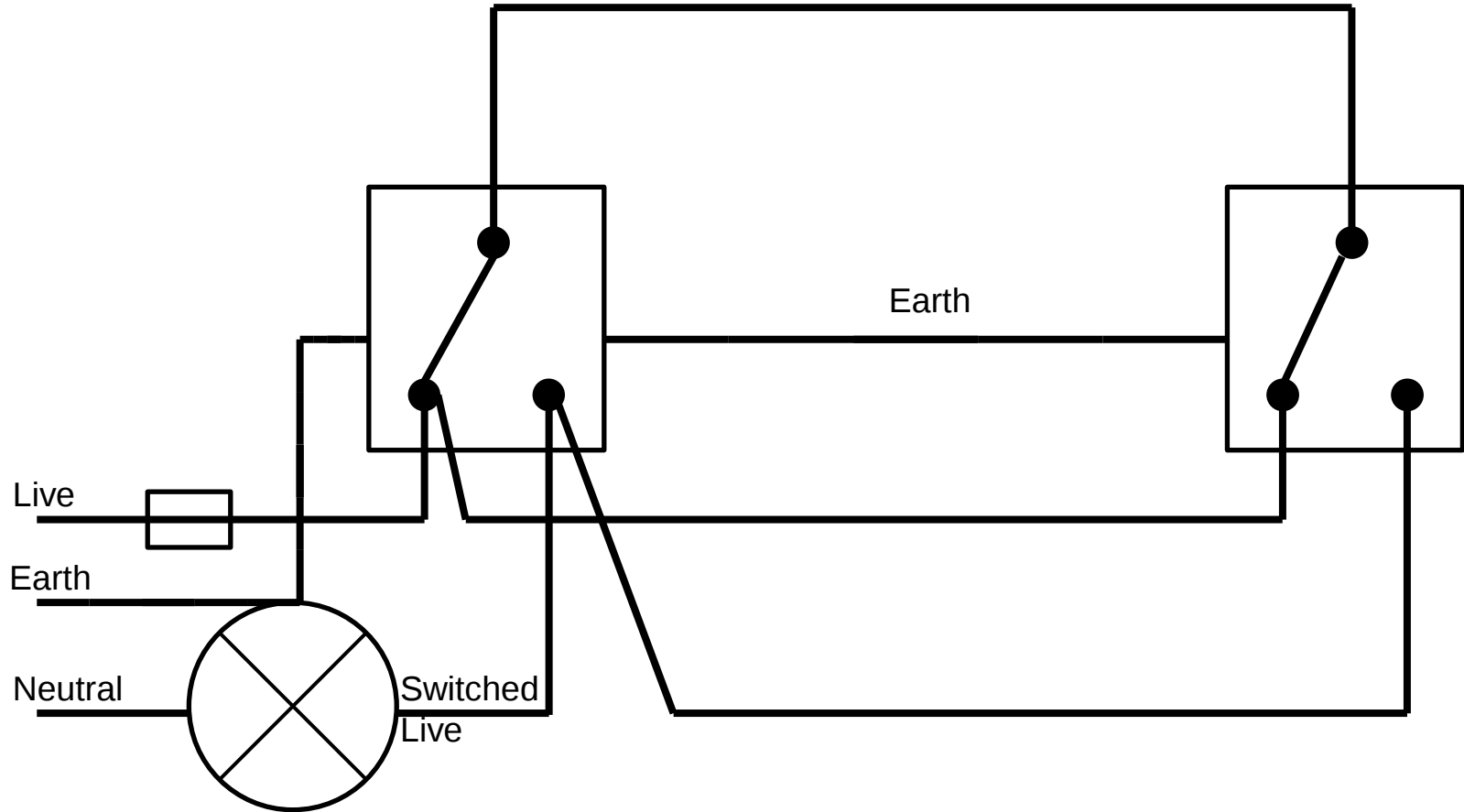


One Way Switching (Wiring Diagram)

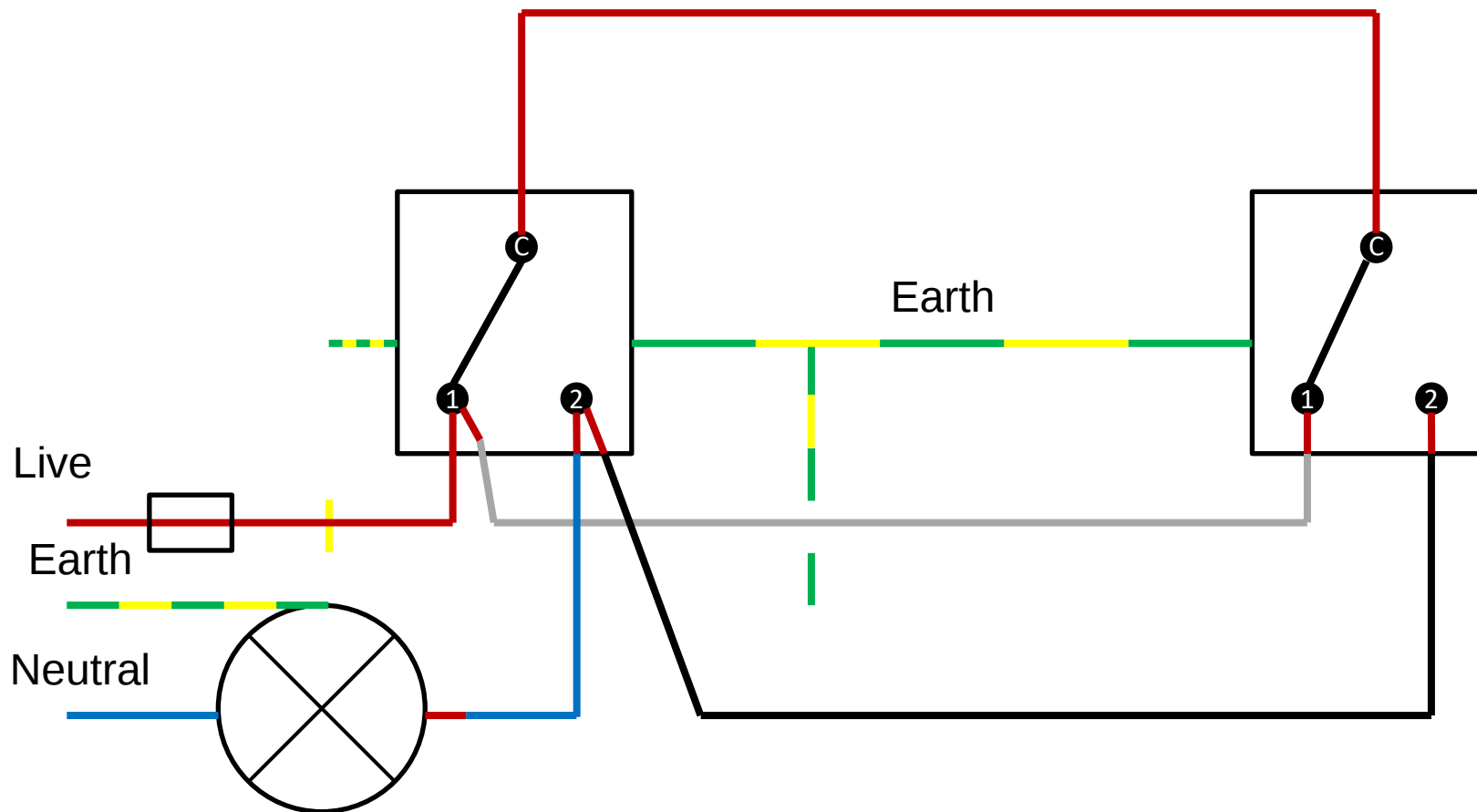


Two Way Switching

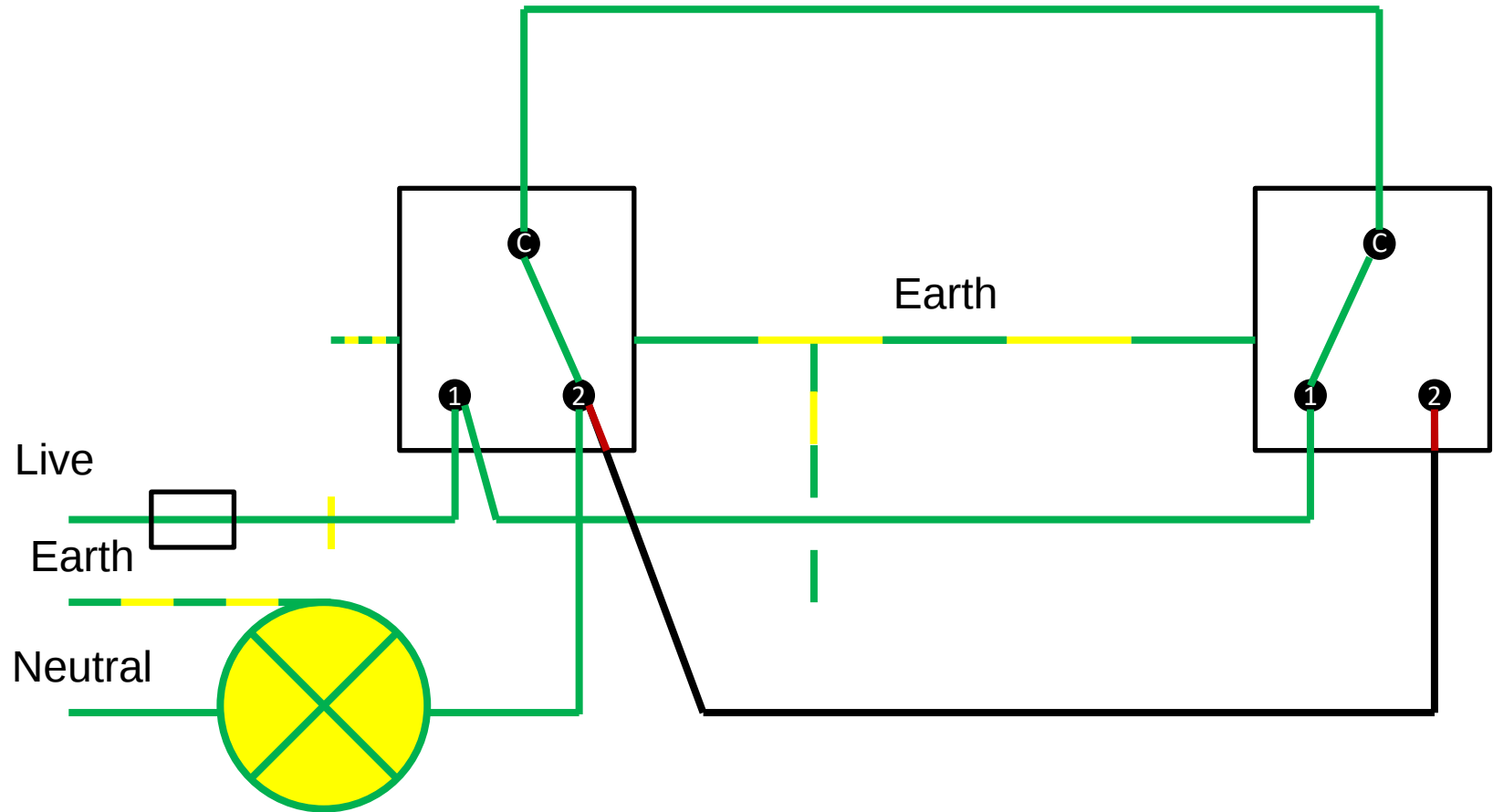


Two Way Switching

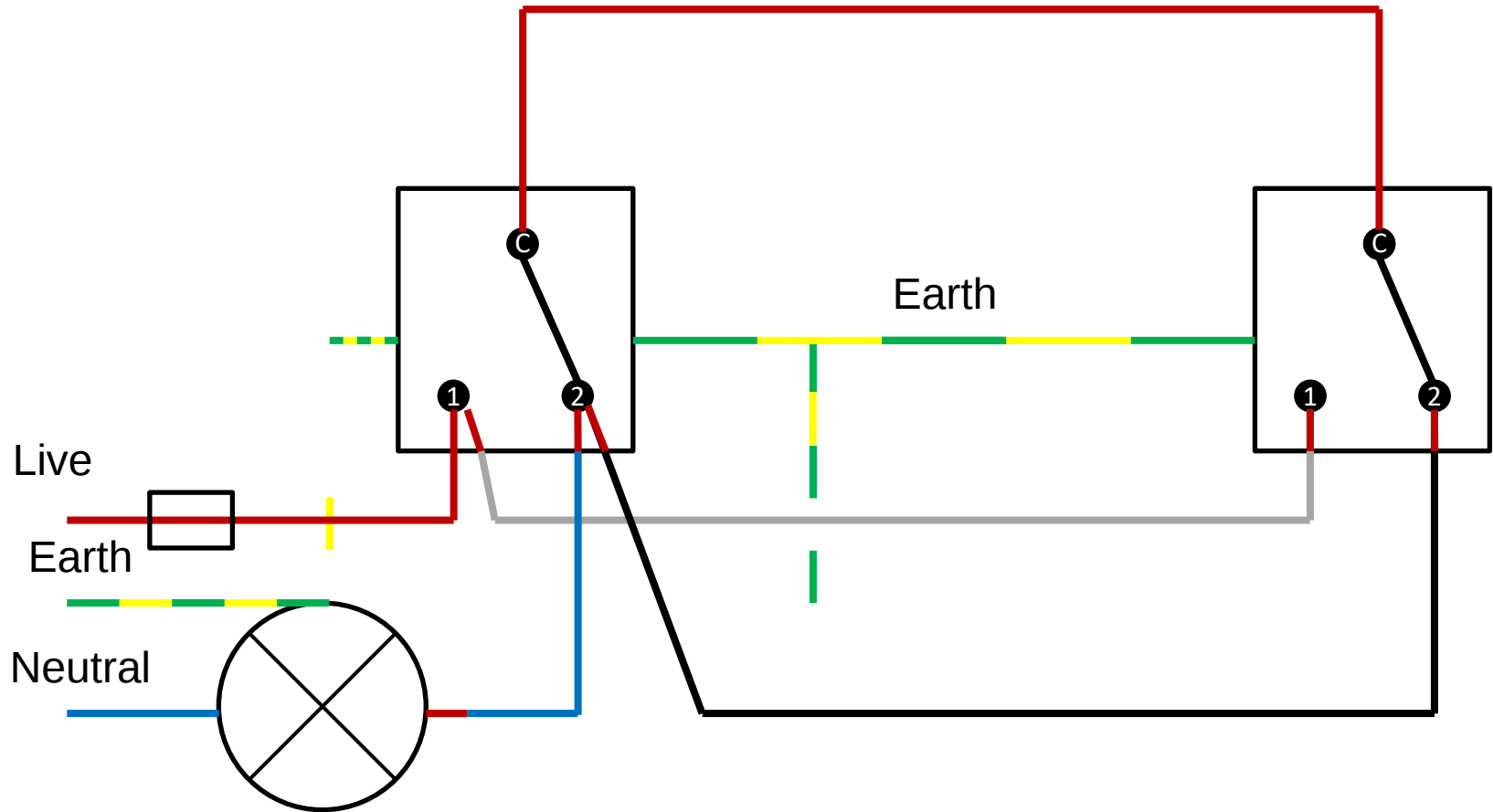


Two Way Switching

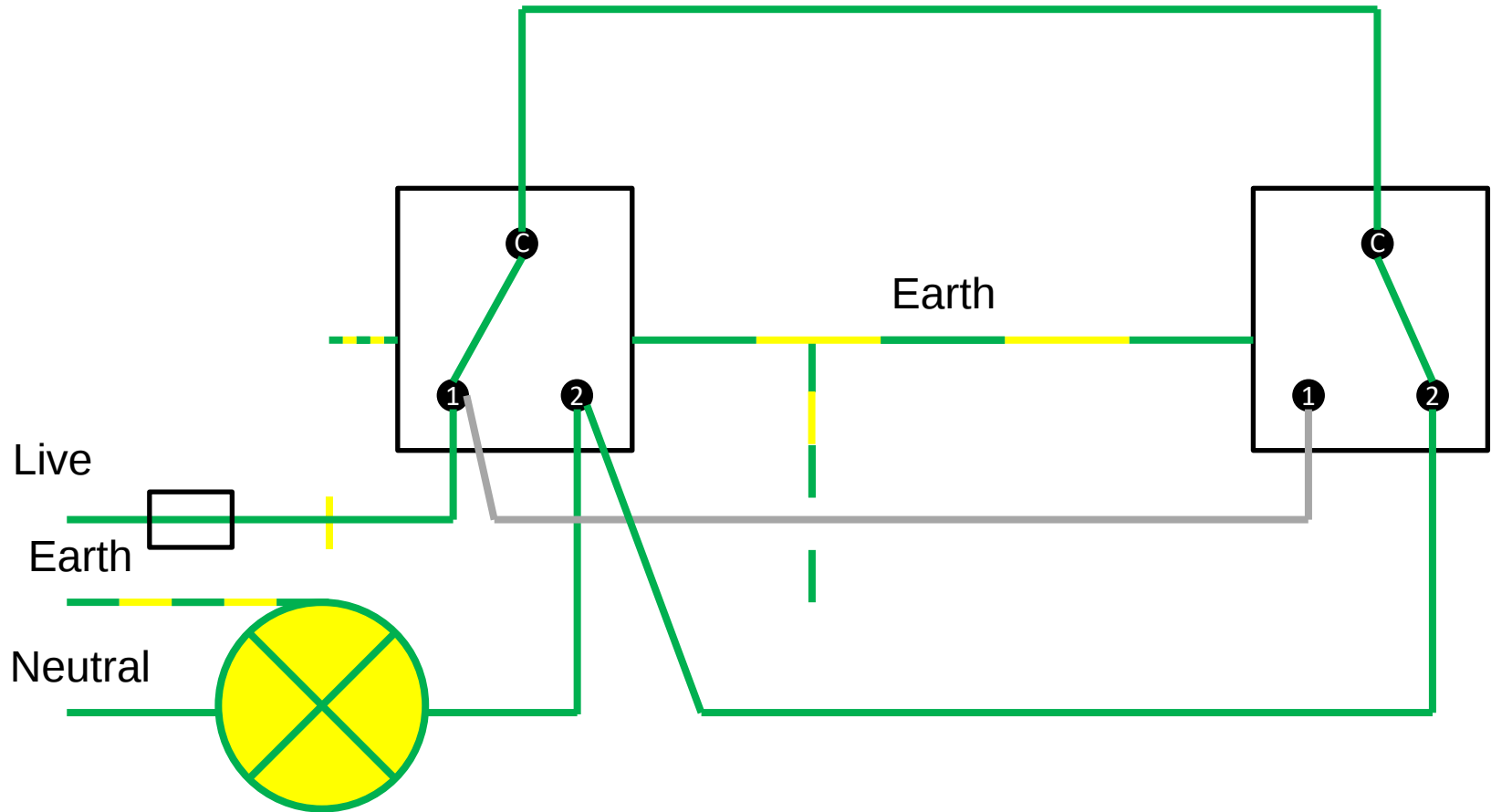


Two Way Switching

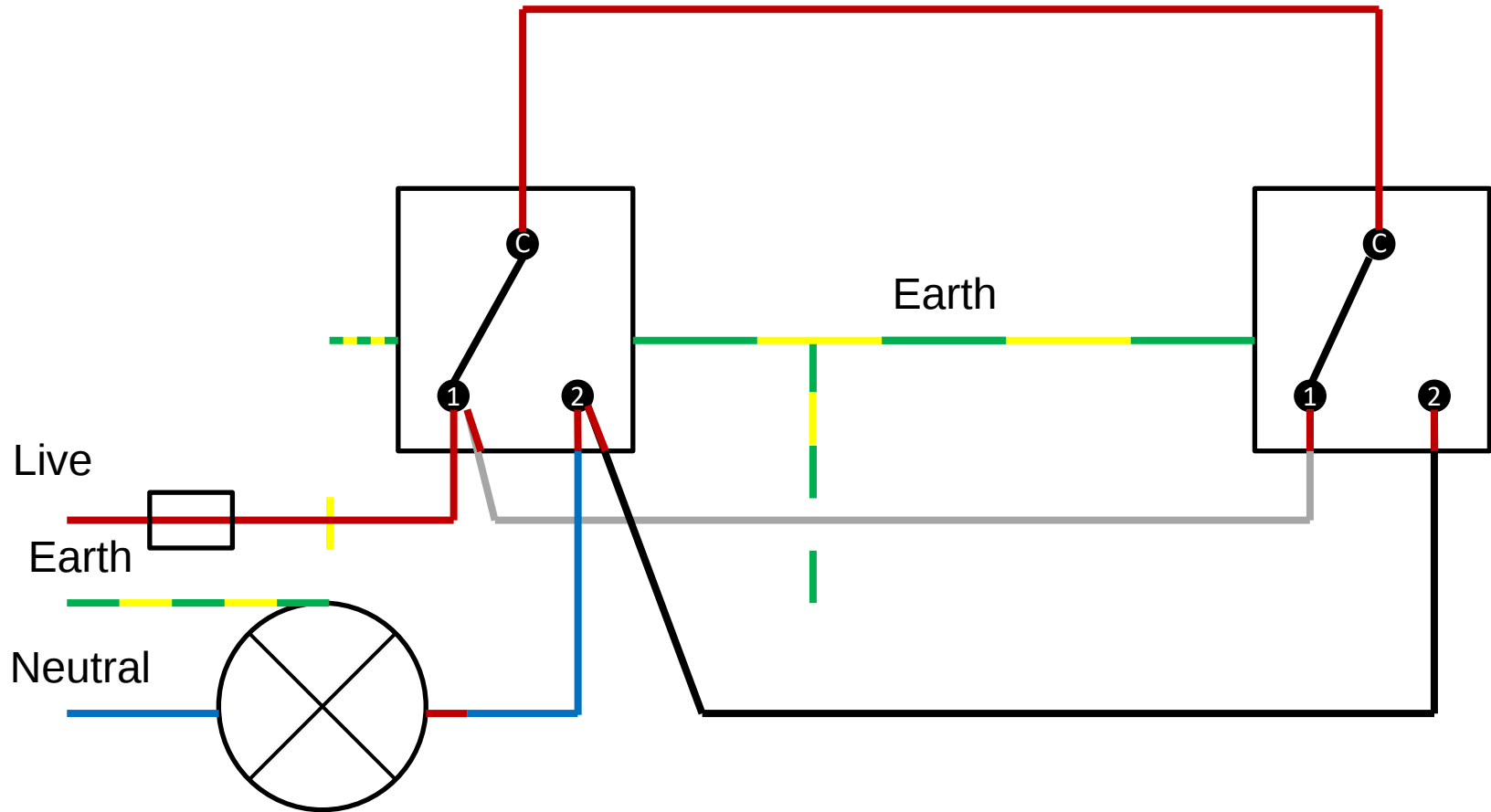


Intermediate Switching (Circuit Diagram)

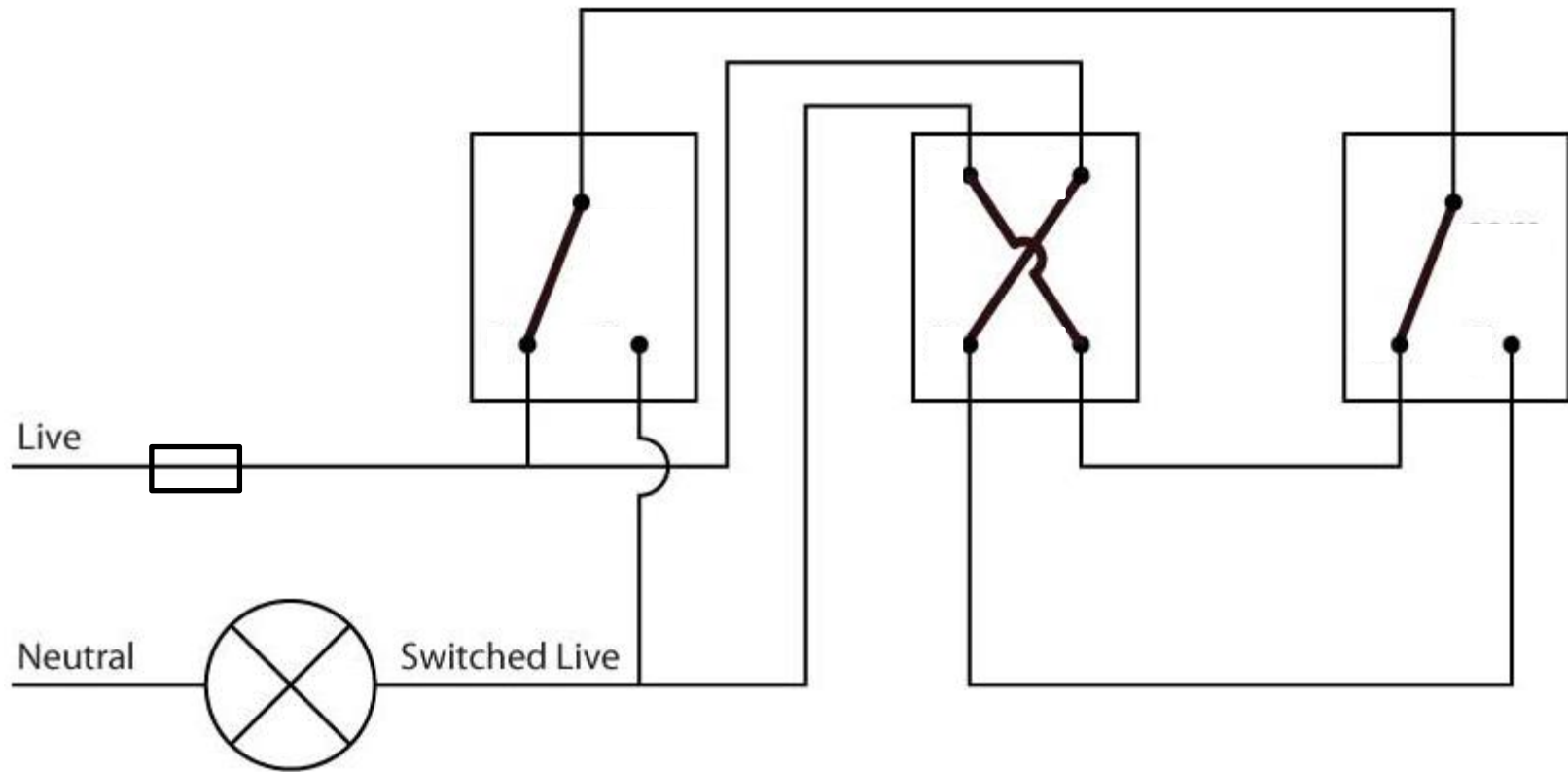


Intermediate Switching (Wiring Diagram)

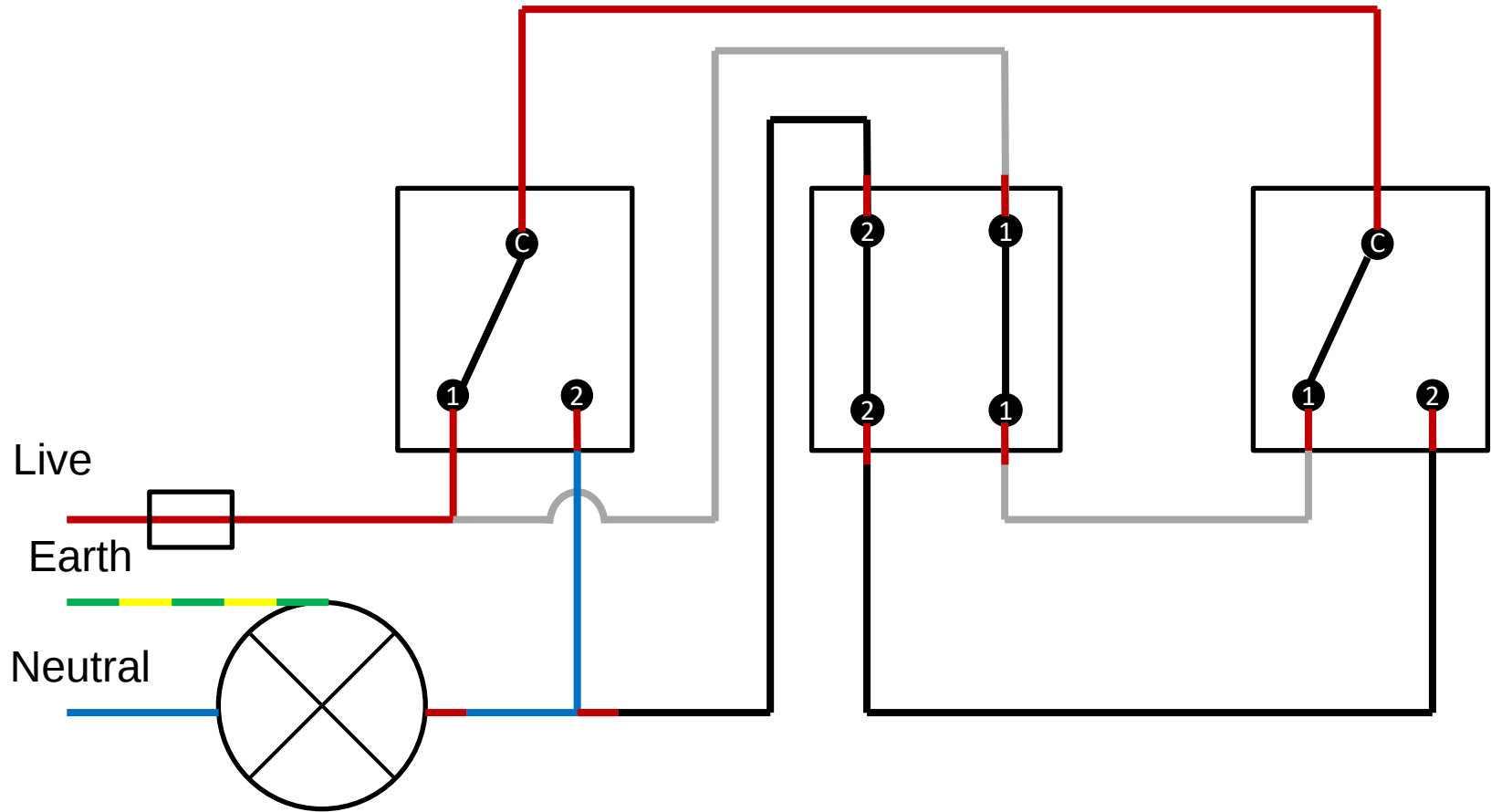


Intermediate Switching

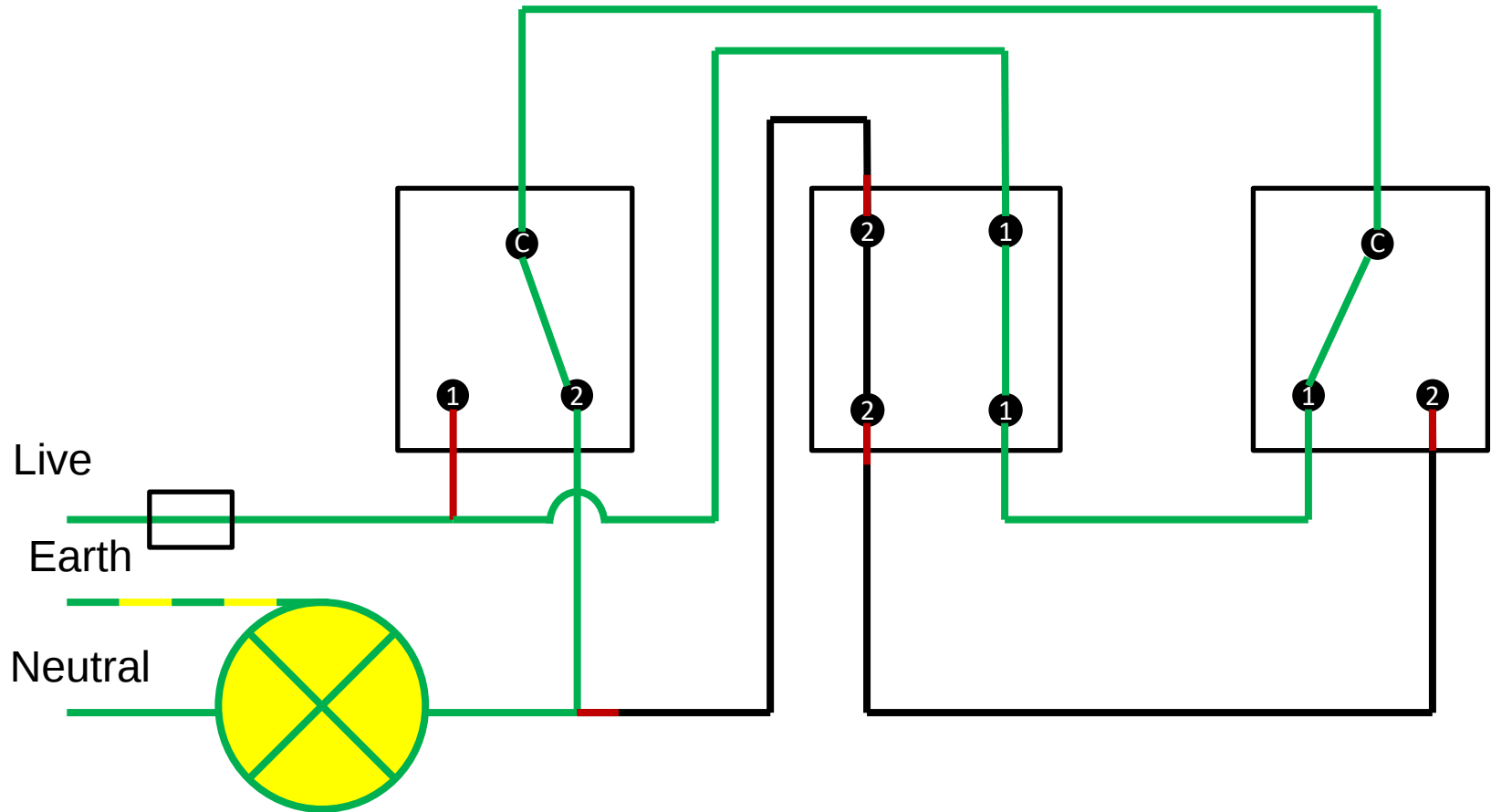


Intermediate Switching

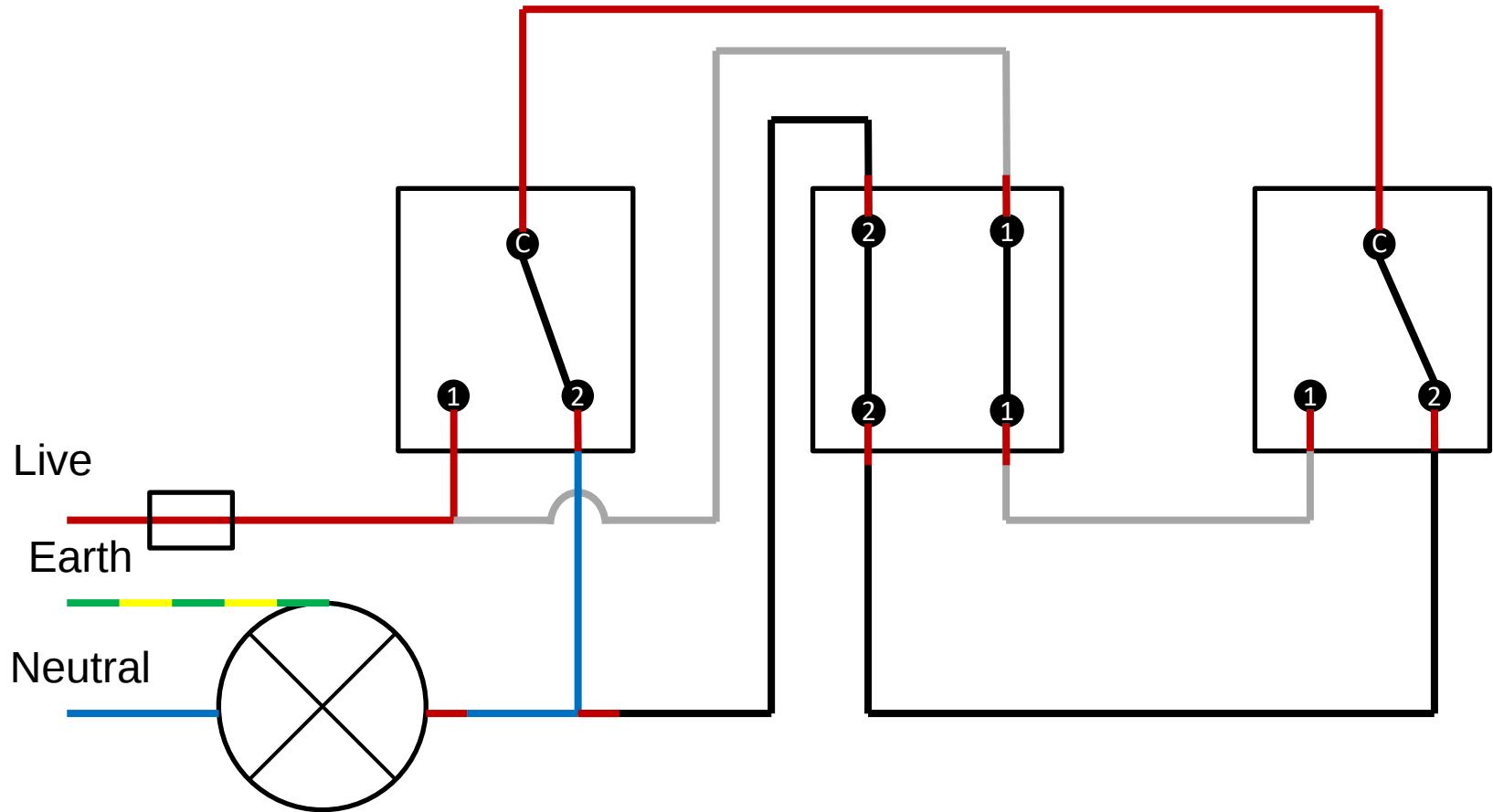


Intermediate Switching

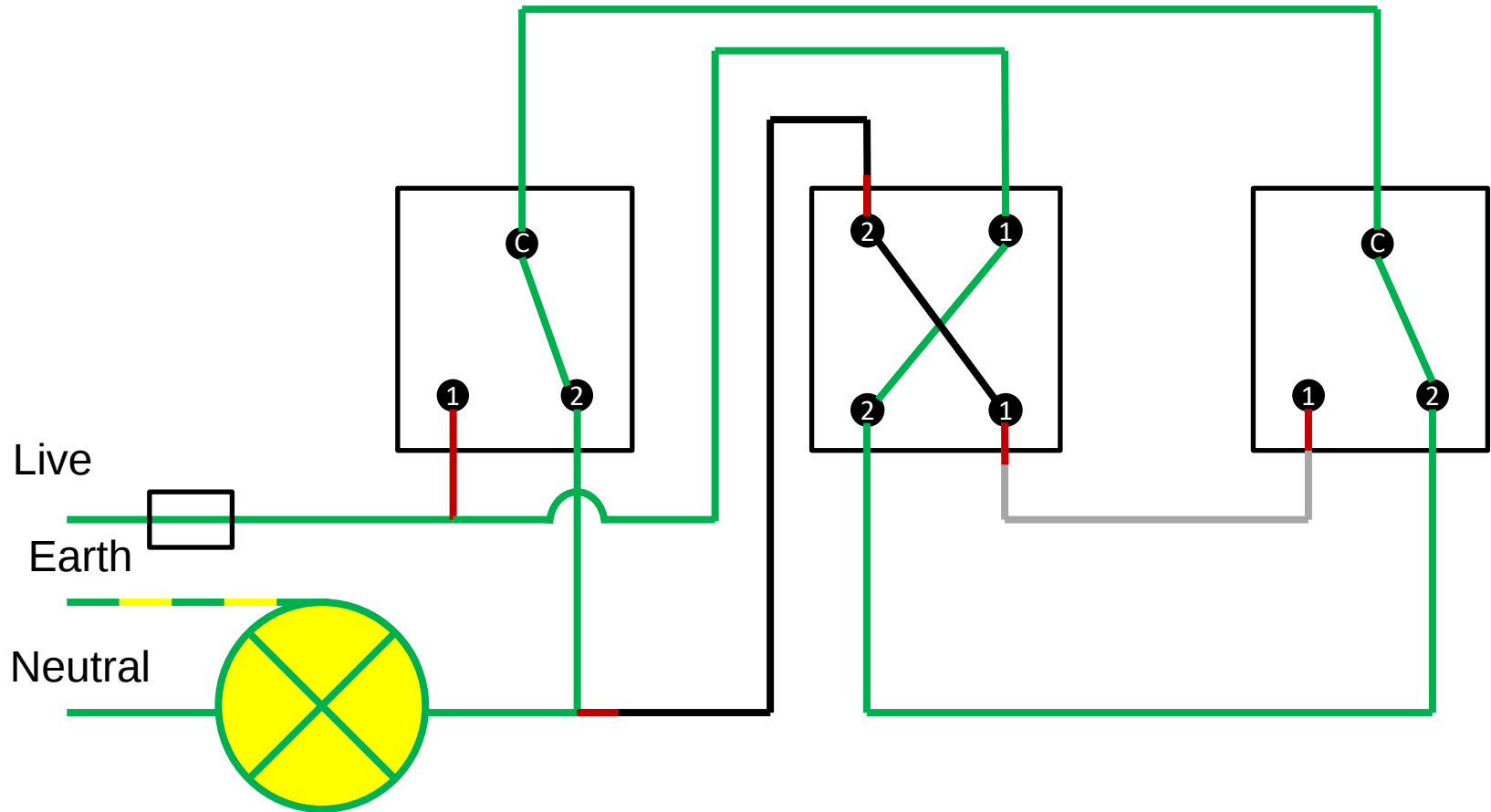

Intermediate Switching

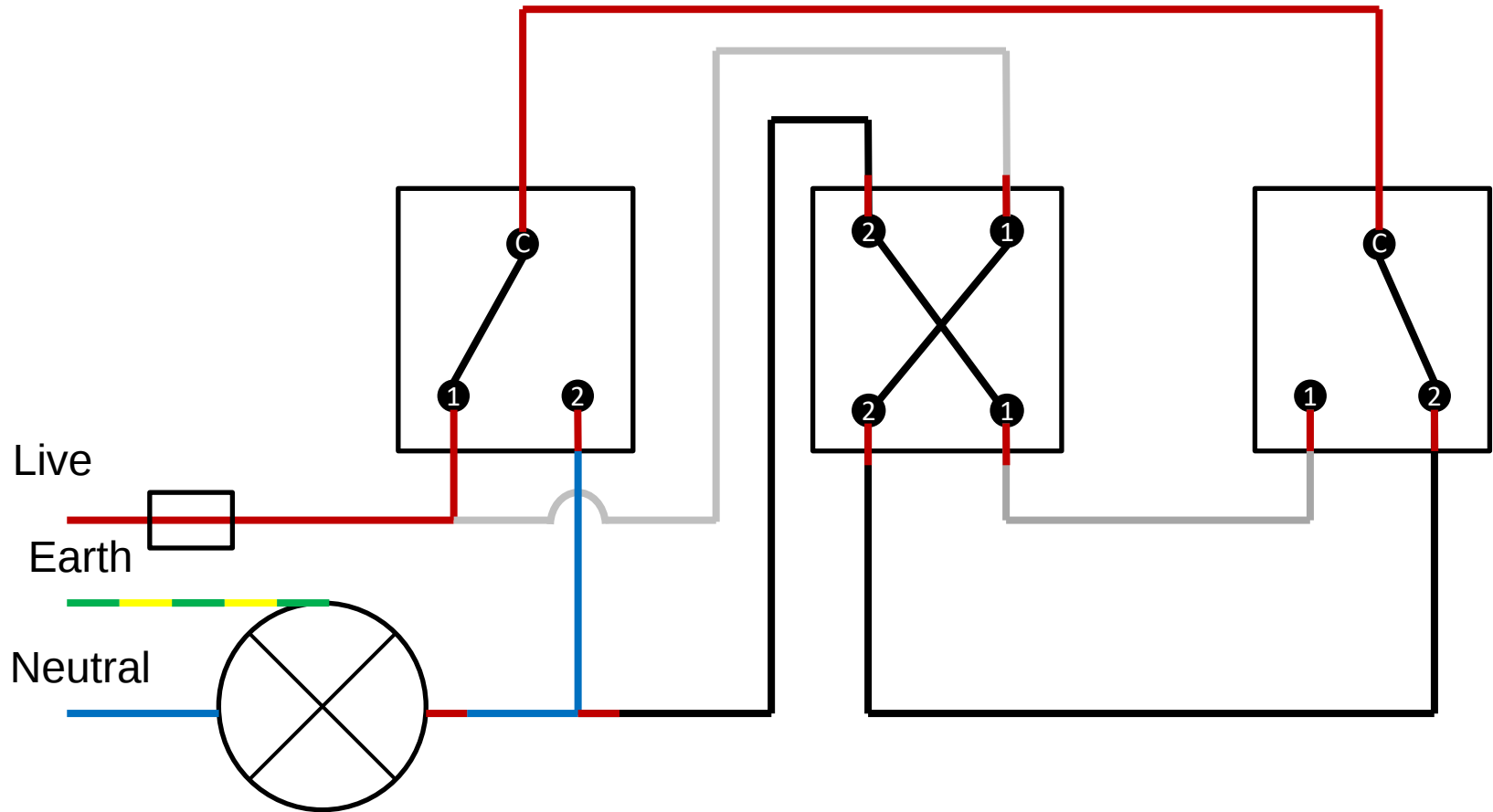

Intermediate Switching

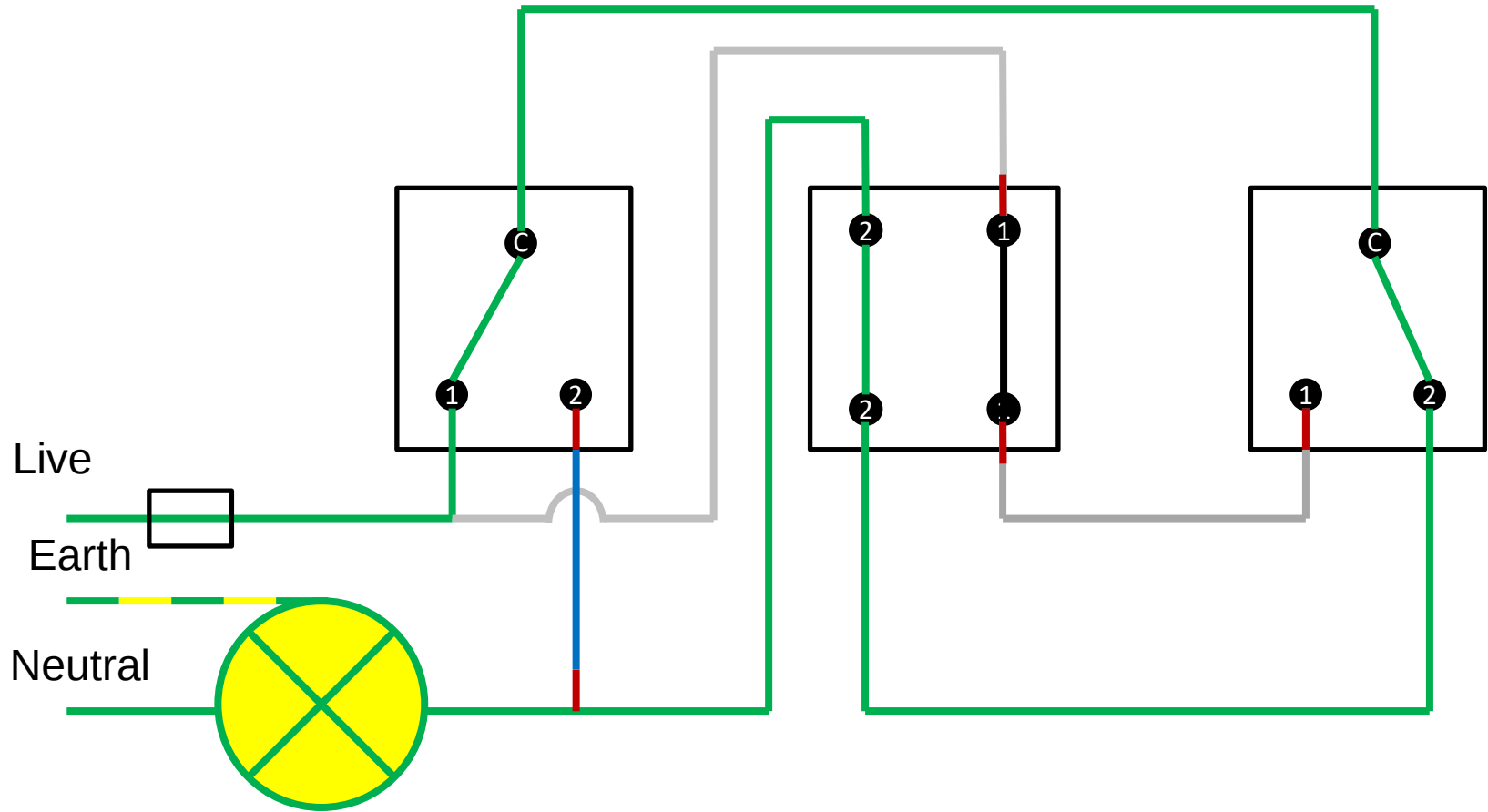

Intermediate Switching

