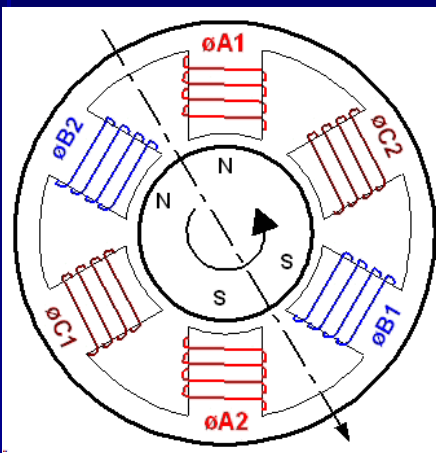


Variable Speed Drives (VSD's)


AC Induction motors (History)

Invented and developed in the early 19th century the Induction motor was manufactured with **fixed** speeds based on the number of poles or pairs of poles **PER PHASE**:




2 Pole Motor
1 Pair

$$N_s = \quad \text{RPM}$$

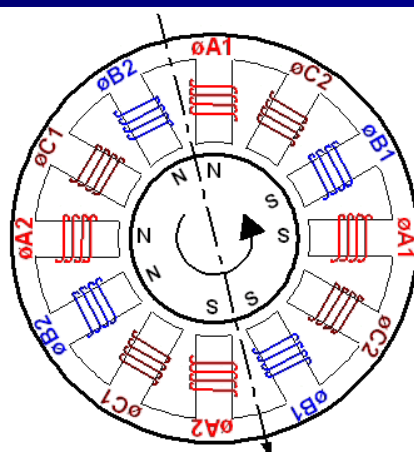

4 Pole Motor
2 Pairs

$$N_s = \quad \text{RPM}$$

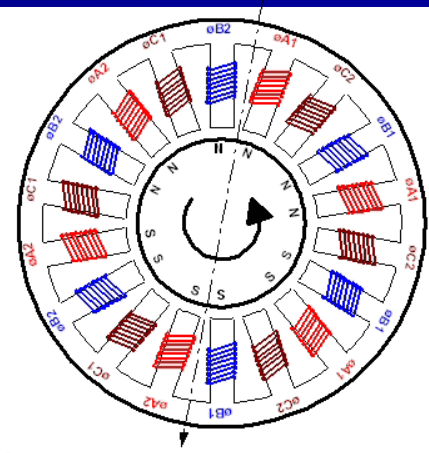

6 Pole Motor
3 Pairs

$$N_s = \quad \text{RPM}$$

Synchronous Speed (N_s)

To calculate the synchronous speed of an Induction motor:

There are two formulae

$$N_s =$$

$$N_s =$$

Asynchronous Speed or Rotor Speed (N_r)

Sometimes referred to as the slip speed

Slip =

And will often be stated as a percentage of synchronous speed: (so multiplied by 100)

So what is the rotor speed of a UK 6 pole motor with 5% Slip?


AC Motor Data Plate

What is the percentage slip of this Induction Motor?


S&C MACHINES Made in U.K.	GEC Small Machines Ltd Alpak INDUCTION MOTOR B.S.5000			
	Size	D90S	No.	LA303 13131
	kW.	1.5	r/min.	2820
			ph.	3 Hz50
	V.	220-240/380-415	A.	5.6/3.2
	Duty type	S1	P.f.	Conn. Δ/Y
	Brg.D.E.	620522	Ins.Class	F
	Brg.N.D.E.	620522	Diag.	55
		Amb °C	Alt.m.	Encl. TPW54
			Mass kg.	0111110

Variable Speed Control of AC Motors

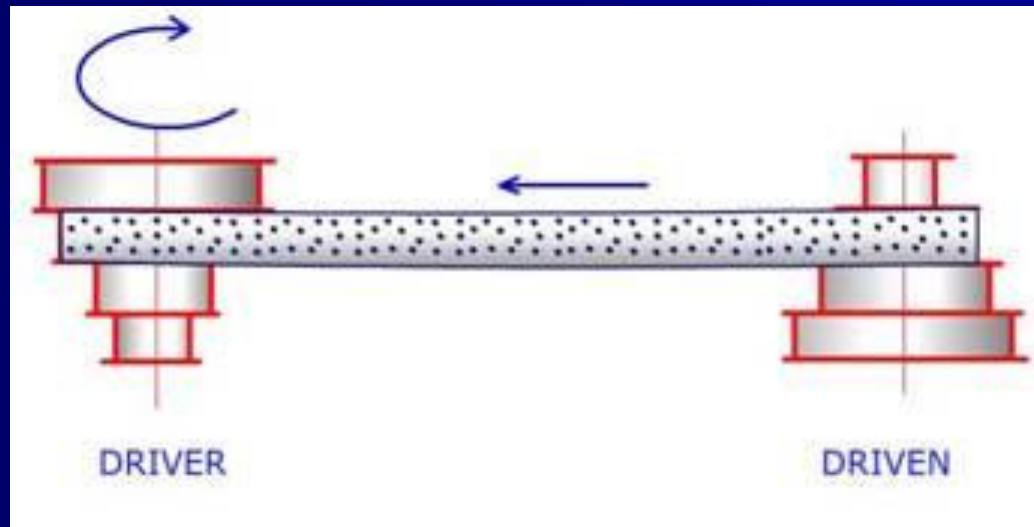
Before the onset of Semiconductors and Micro-electronics variable speed control of AC Induction motors was limited to mechanical solutions



Variable Speed Control of AC Motors

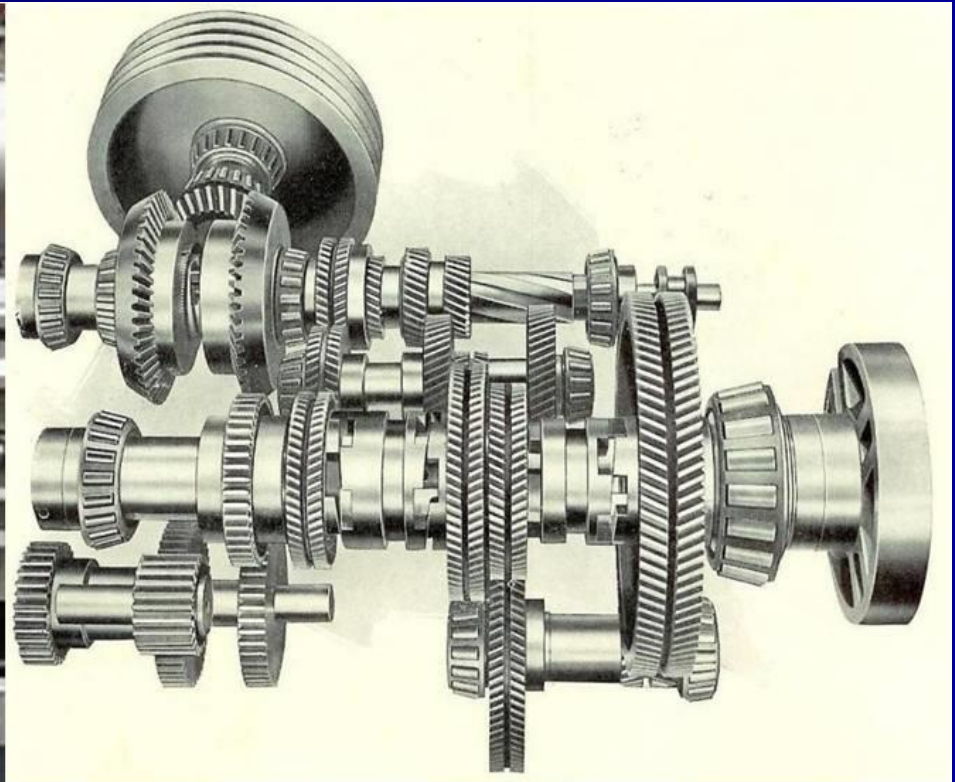

Variable Speed Control AC Motors

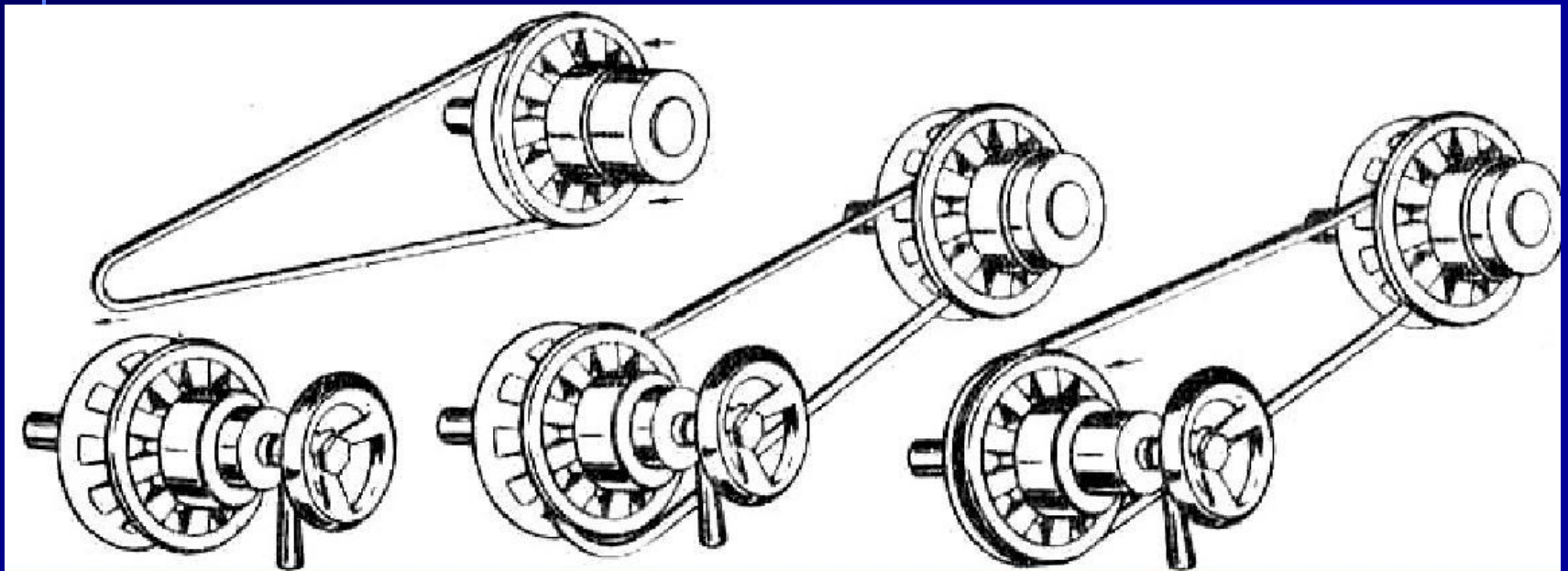


Electrical Speed Control




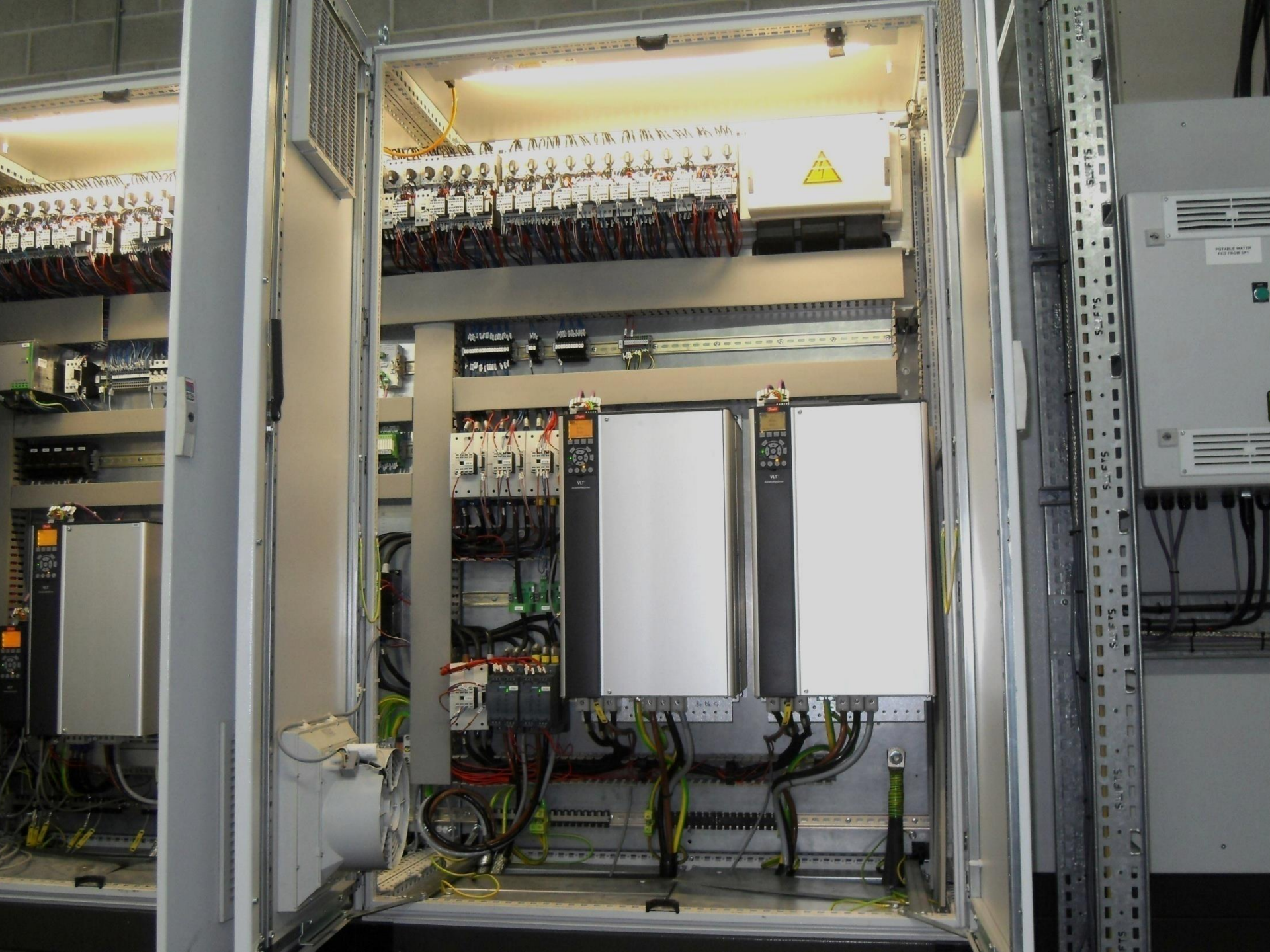Variable speed (frequency) drives/ inverters





Block Diagram

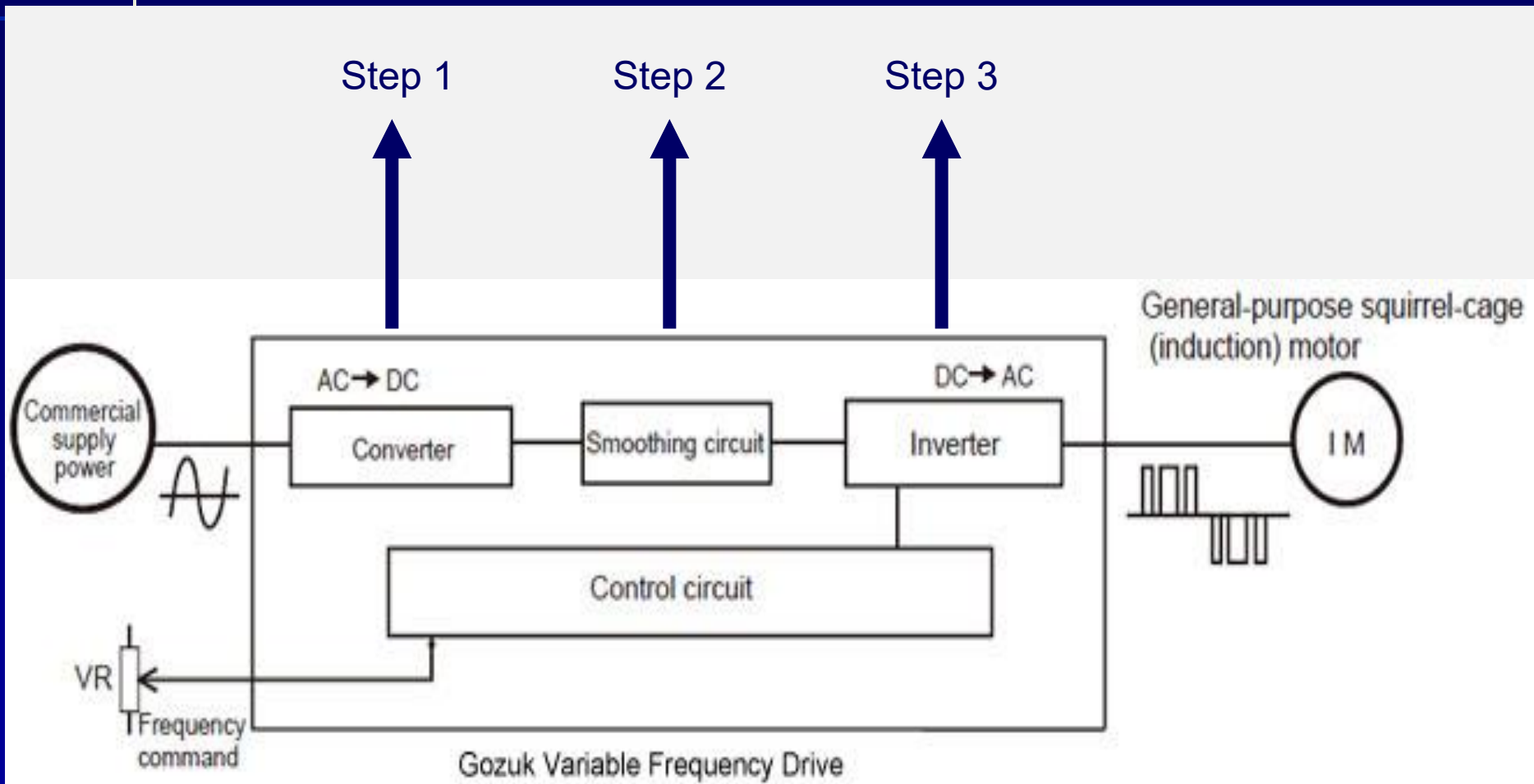

Step 1

How do you change Single
Phase AC to DC?

Single Phase AC to DC?

L _____ +

N _____ -

Step 1

How do you change Three
Phase AC to DC?

Three Phase AC to DC?

L1 _____

_____ +

L2 _____

L3 _____

_____ -


Step 2

How do you smooth
Rippled DC?


Step 3

How do you change DC back into Single Phase AC?

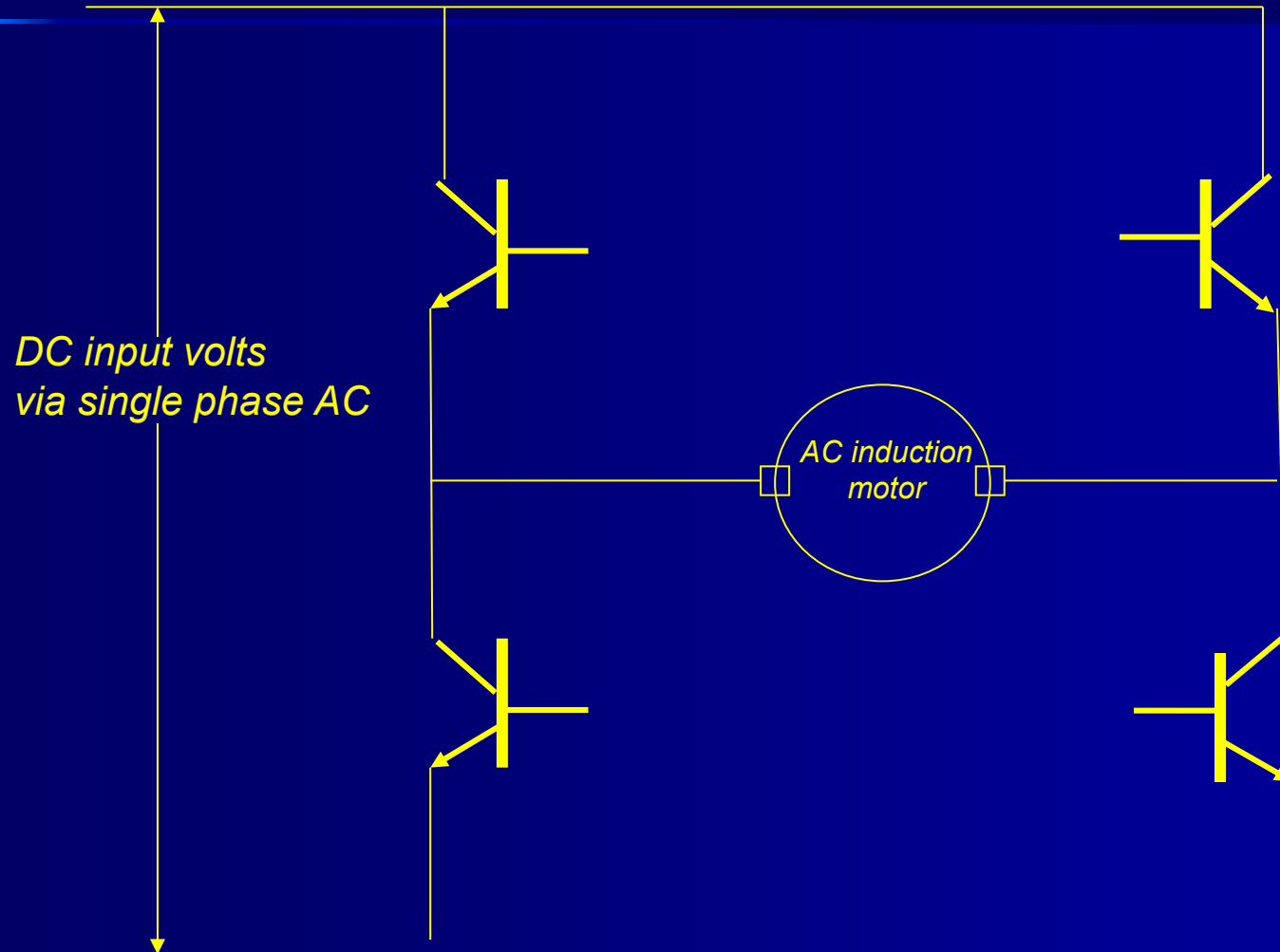
Inverter circuit for single – phase output



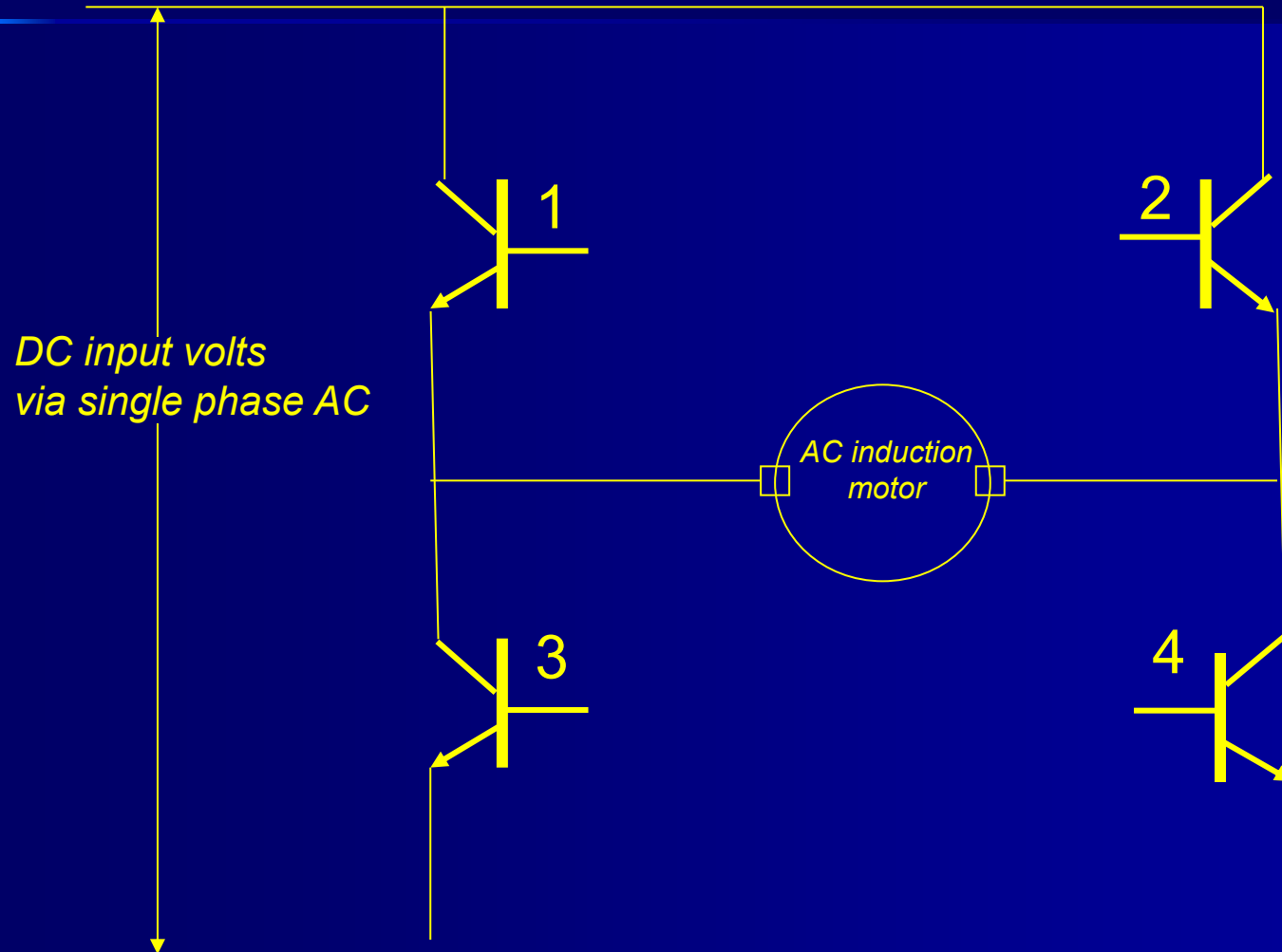Inverter circuit for single – phase output



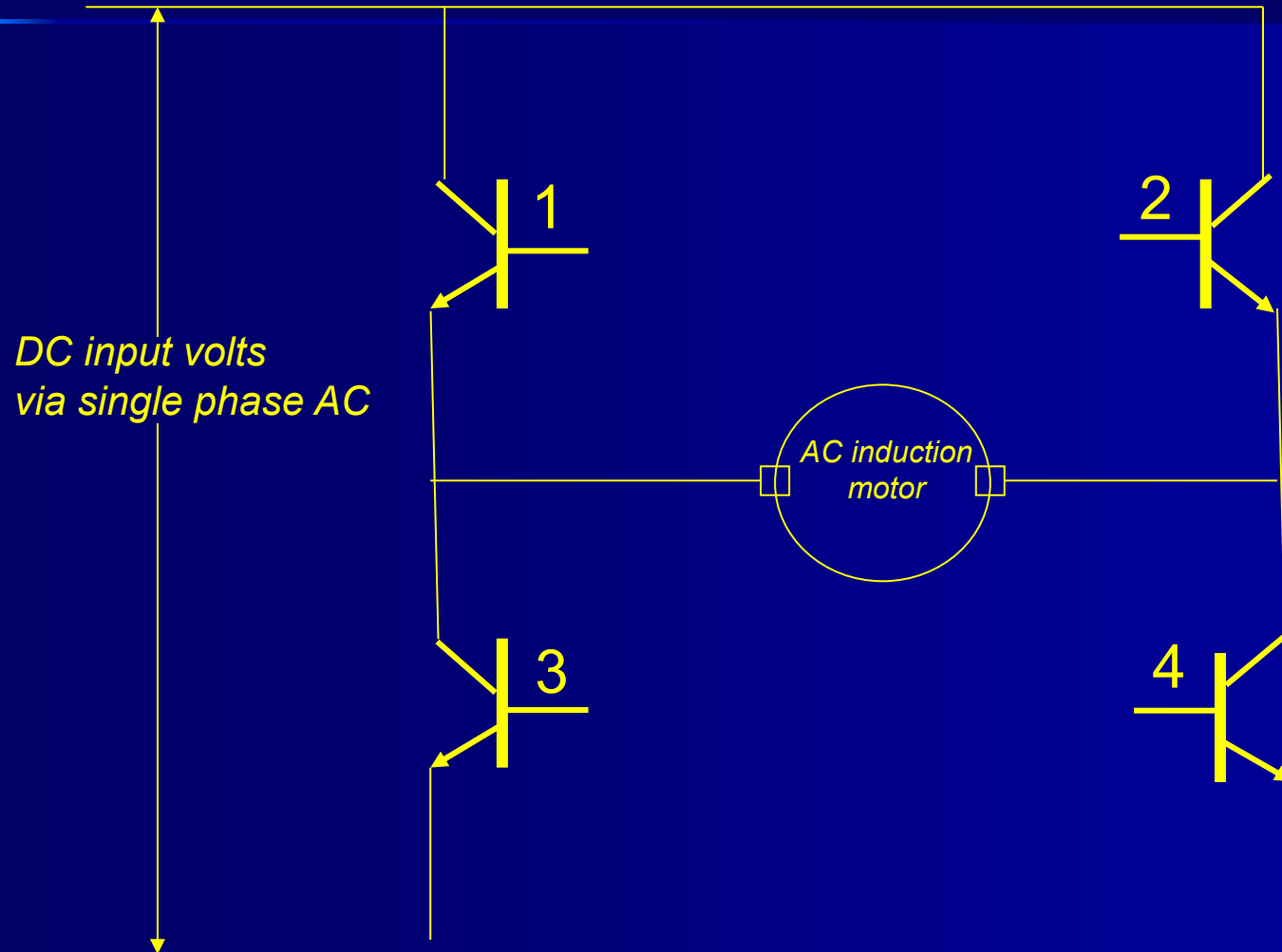
Inverter circuit for single – phase output




Step 3

How do you change DC into
Three Phase AC?


Inverter circuit for 3 – phase output

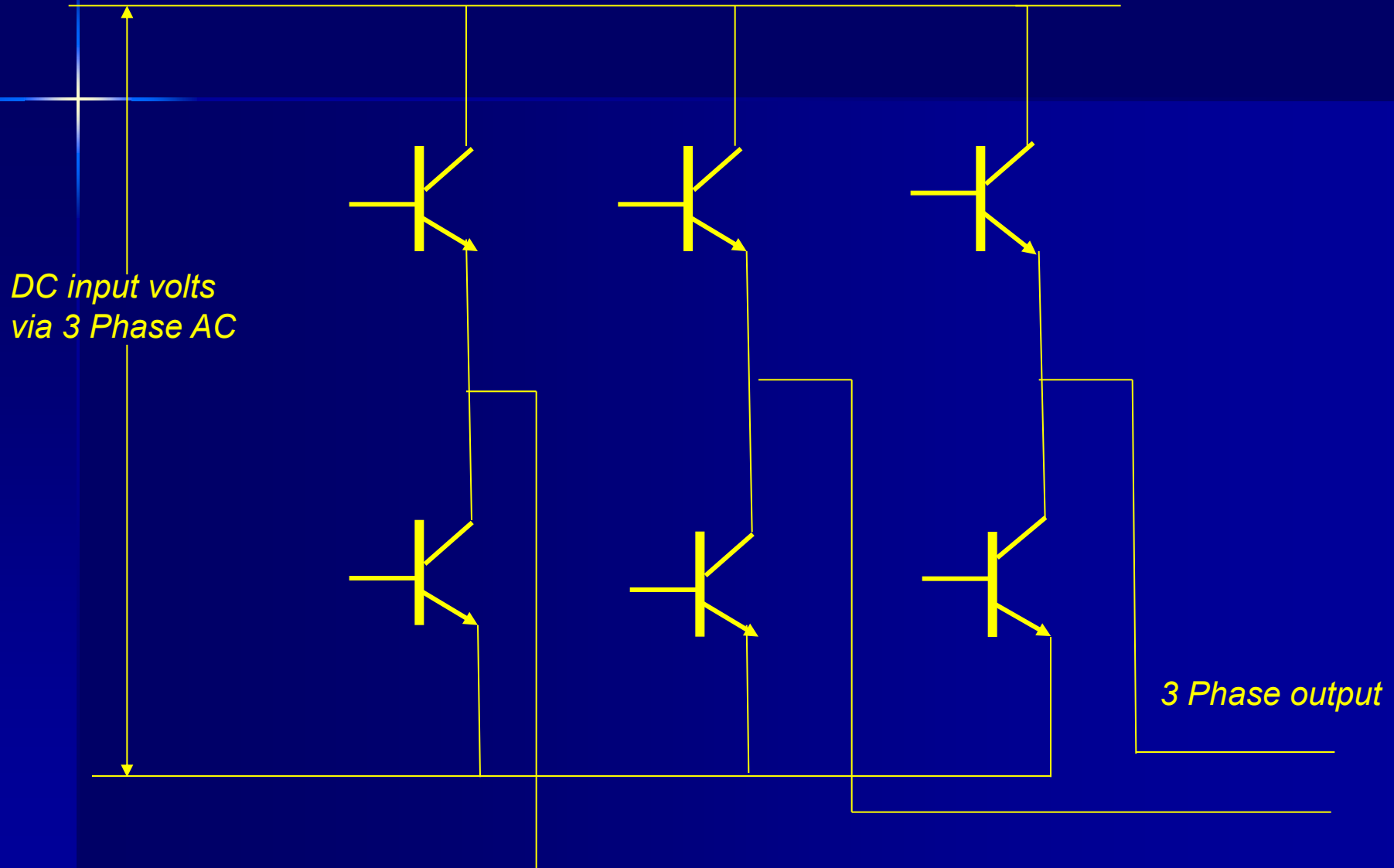


Inverter circuit for 3 – phase output

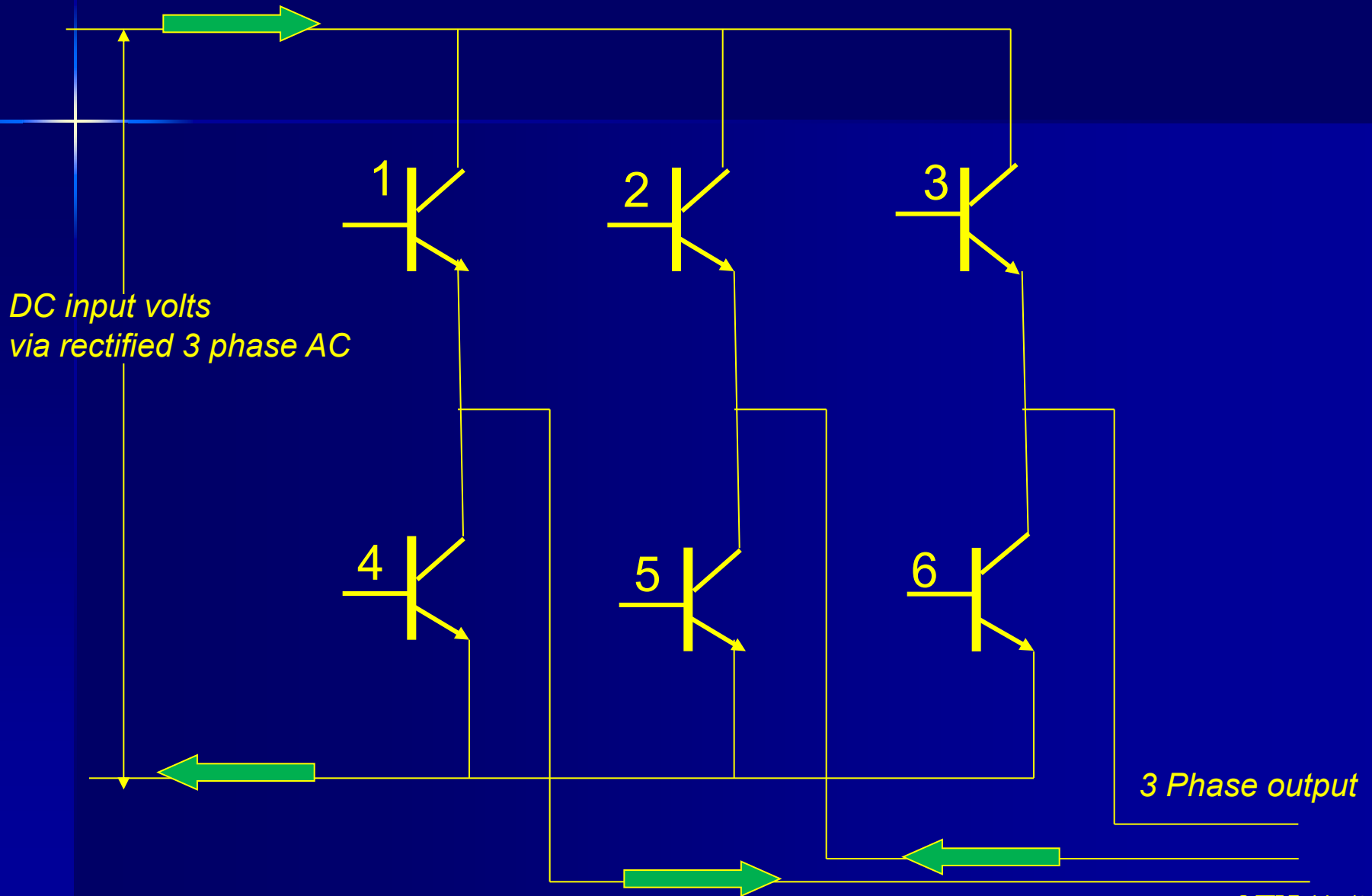


Inverter circuit for 3 – phase output

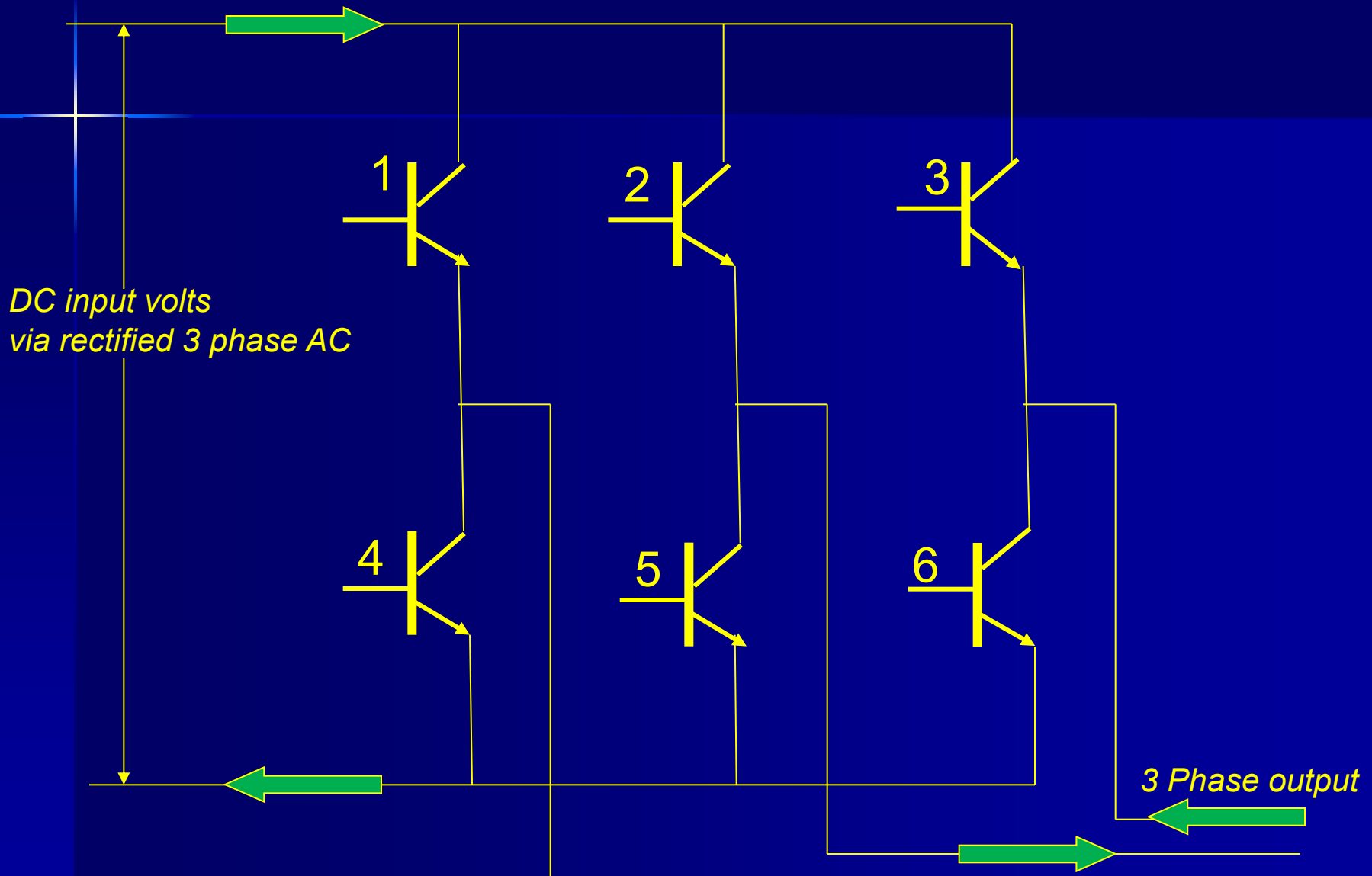


Inverter circuit for 3 – phase output

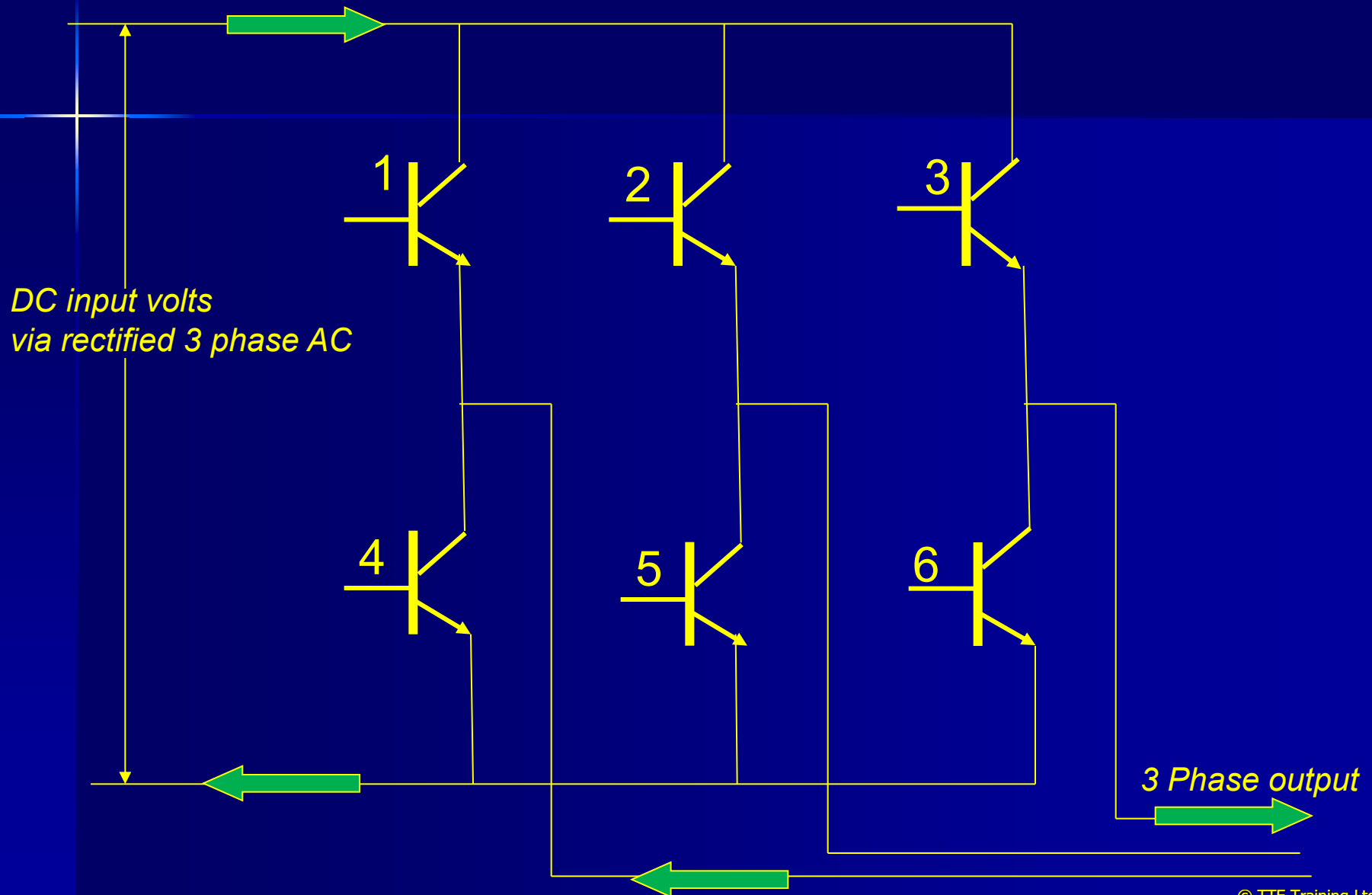

Inverter circuit for 3 – phase output

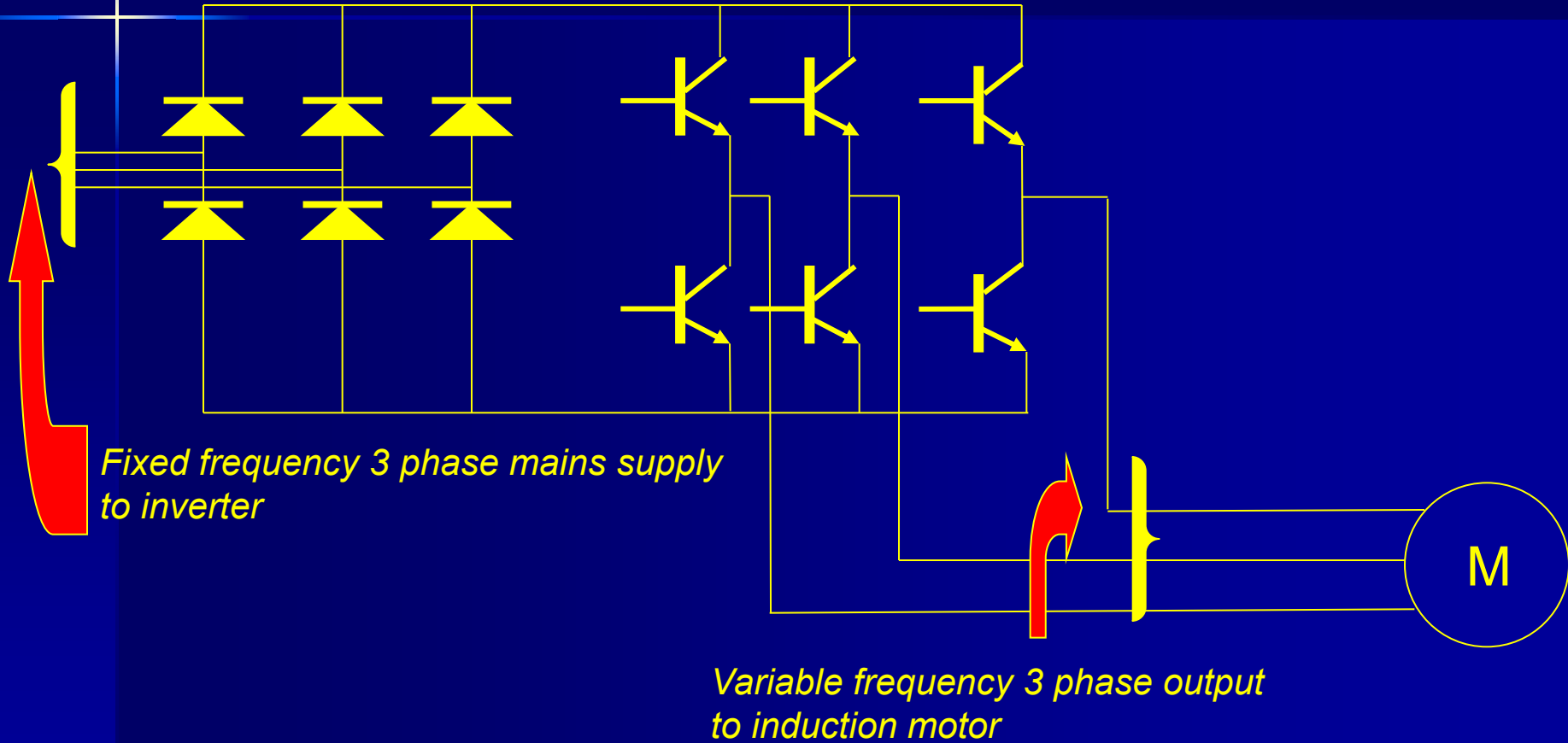


AC Drive Main Circuit

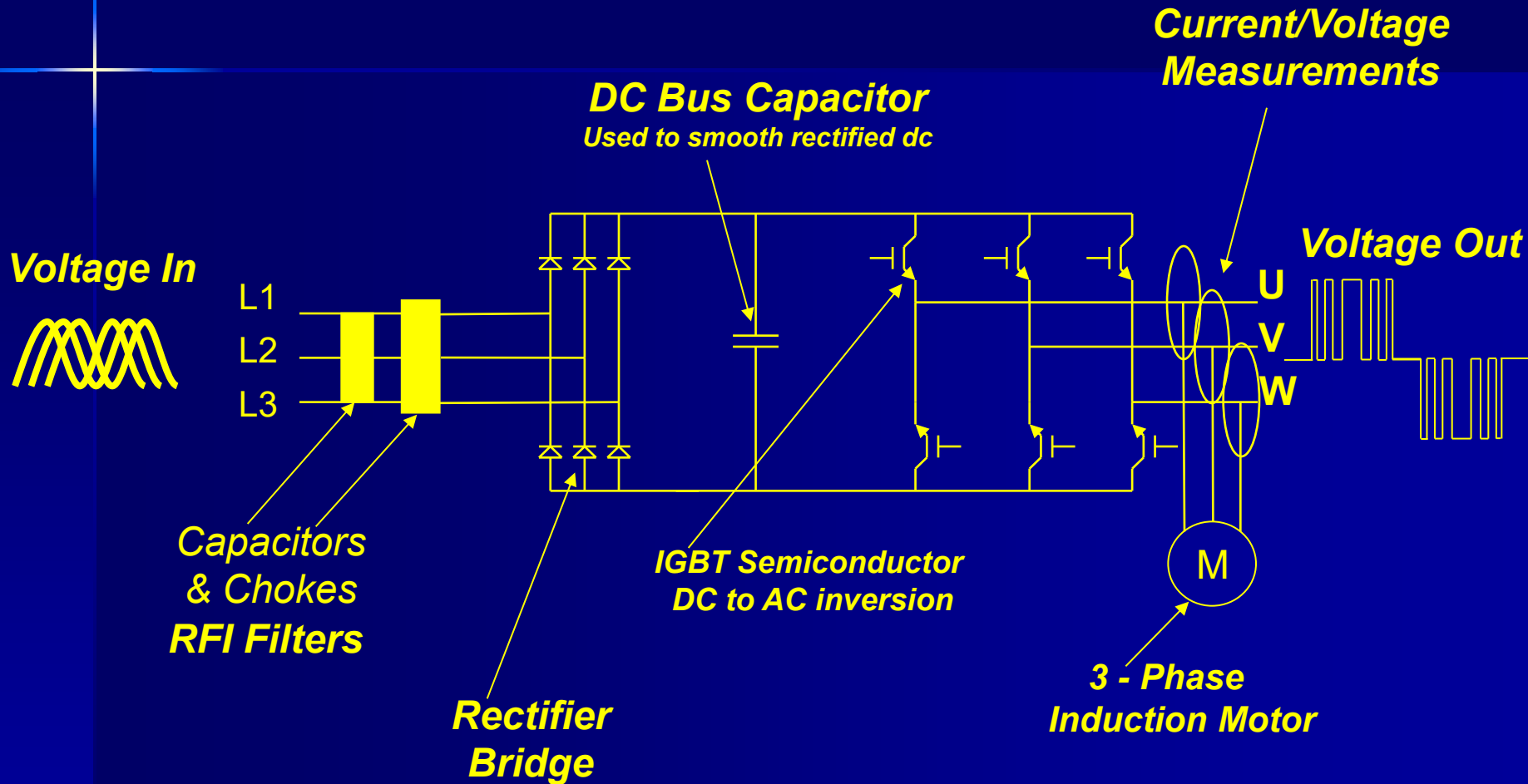


Pulse Width Modulation (PWM)

Varying the frequency

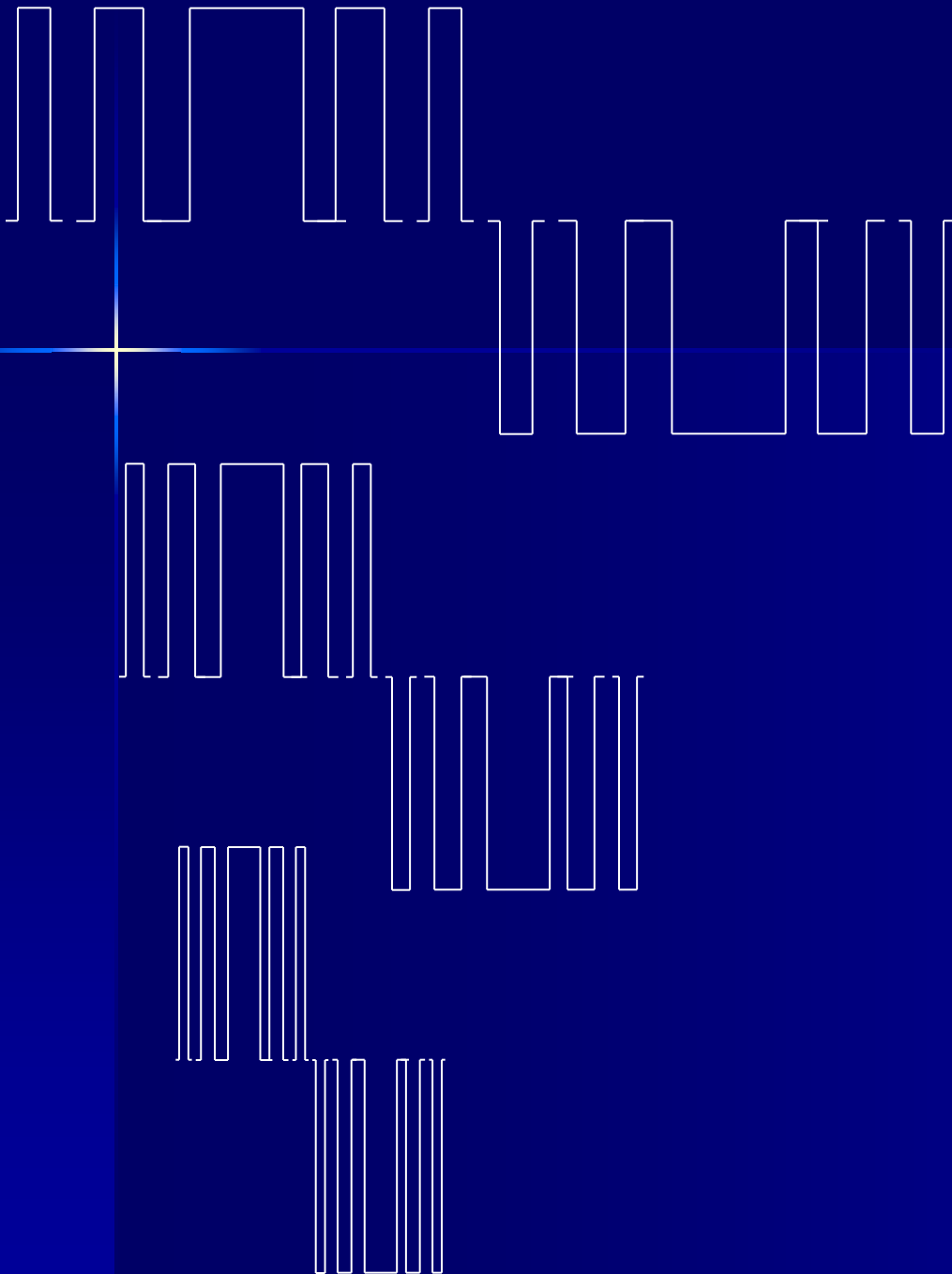


Eurotherm 601 VSD

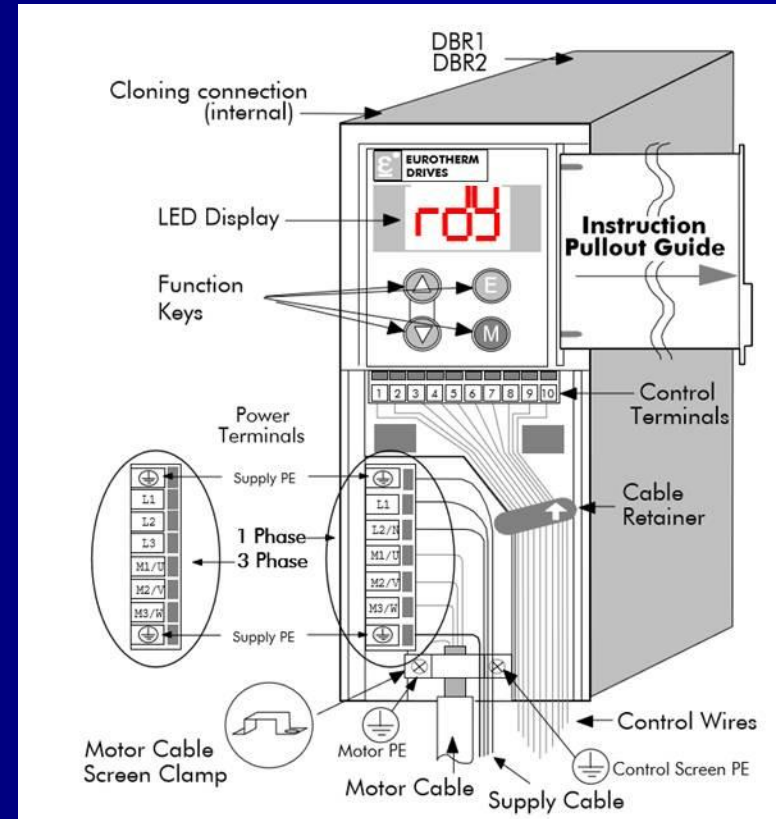

Example Variable Speed Control Timing diagram



Clockwise / Forward

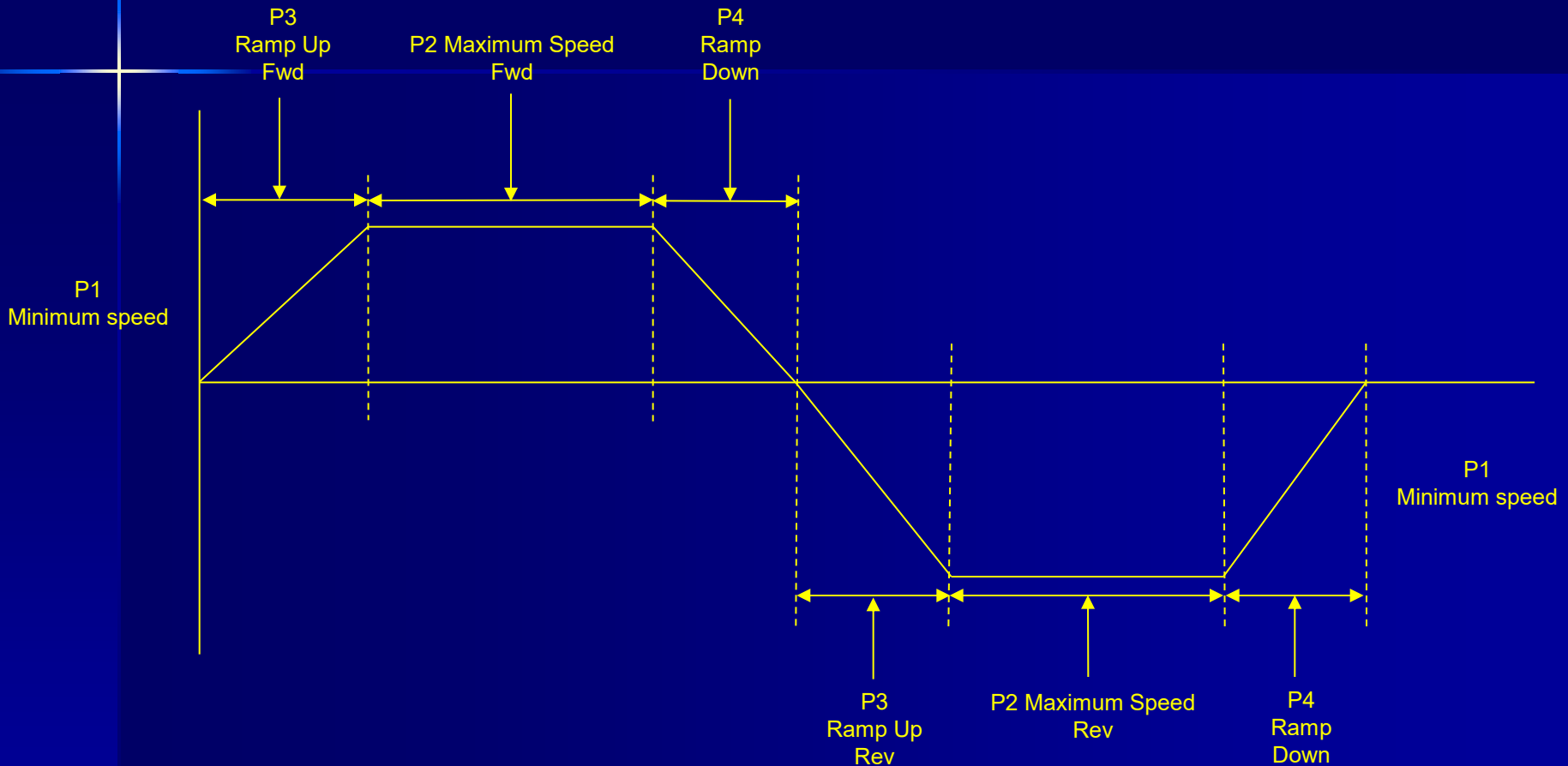

Anti-Clockwise / Reverse

Parameter	Translation	Description	Range	Factory Default
P1	Minimum Speed	The minimum frequency at which the inverter will run	0 – 240 Hz	0 - Hz
P2	Maximum Speed	The maximum frequency at which the inverter will run	0 – 240 Hz	50 / 60 Hz
P3	Ramp Up Time	The time for the inverter output frequency to ramp up from zero to maximum speed	0.1 – 999s	10s
P4	Ramp Down Time	The time for the inverter output frequency to ramp up from maximum speed to zero	0.1 – 999s	10s
P11	Stopping Mode	Controlled stopping of motor	Ramp Coast Injection	Ramp

<i>P1</i> <i>0 – 240 Hz</i>	<i>P2</i> <i>0 – 240 Hz</i>	<i>P3</i> <i>0.1 – 999s</i>	<i>P4</i> <i>0.1 – 999s</i>	<i>P11</i> <i>Ramp = 0</i> <i>Coast = 1</i> <i>Injection = 2</i>
<i>Minimum Speed</i>	<i>Maximum Speed</i>	<i>Ramp Up Time</i>	<i>Ramp Down Time</i>	<i>Stopping Mode</i>
<i>10</i>	<i>100</i>	<i>15</i>	<i>10</i>	<i>1</i>
<i>25</i>	<i>75</i>	<i>25</i>	<i>15</i>	<i>0</i>
<i>2</i>	<i>150</i>	<i>45</i>	<i>30</i>	<i>0</i>


MMI Status Level

rdy

Display Value Level

**Diagnostic values
Display only**

Title Level	P15	d1	d2	d3	P1	P2	P15
------------------------	-----	----	----	----	----	----	----	----	----	-----

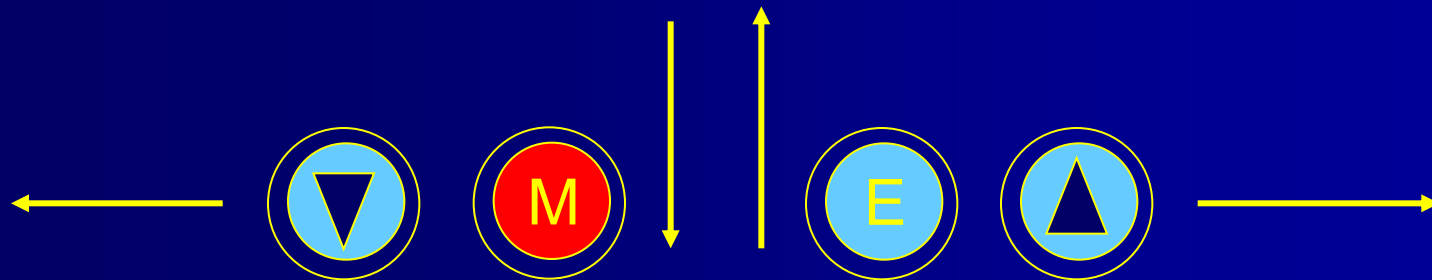

4 Function Keys

Current Parameter values are displayed

Use   to increase / decrease

Parameter values